

Essentials of MOSFETs

# Unit 1: Transistors and Circuits


## Lecture 1.2: Digital Circuits

**Mark Lundstrom**


lundstro@purdue.edu  
Electrical and Computer Engineering  
Purdue University  
West Lafayette, Indiana USA

# Applications of MOSFETs


symbol

 

**digital**

 


analog

 


# N-MOSFET as a switch

---

N-MOSFET  
symbol

 


switch

 


# P-MOSFET as a switch

---

P-MOSFET  
symbol

 


switch

 


# CMOS Inverter


---

 

# CMOS inverter

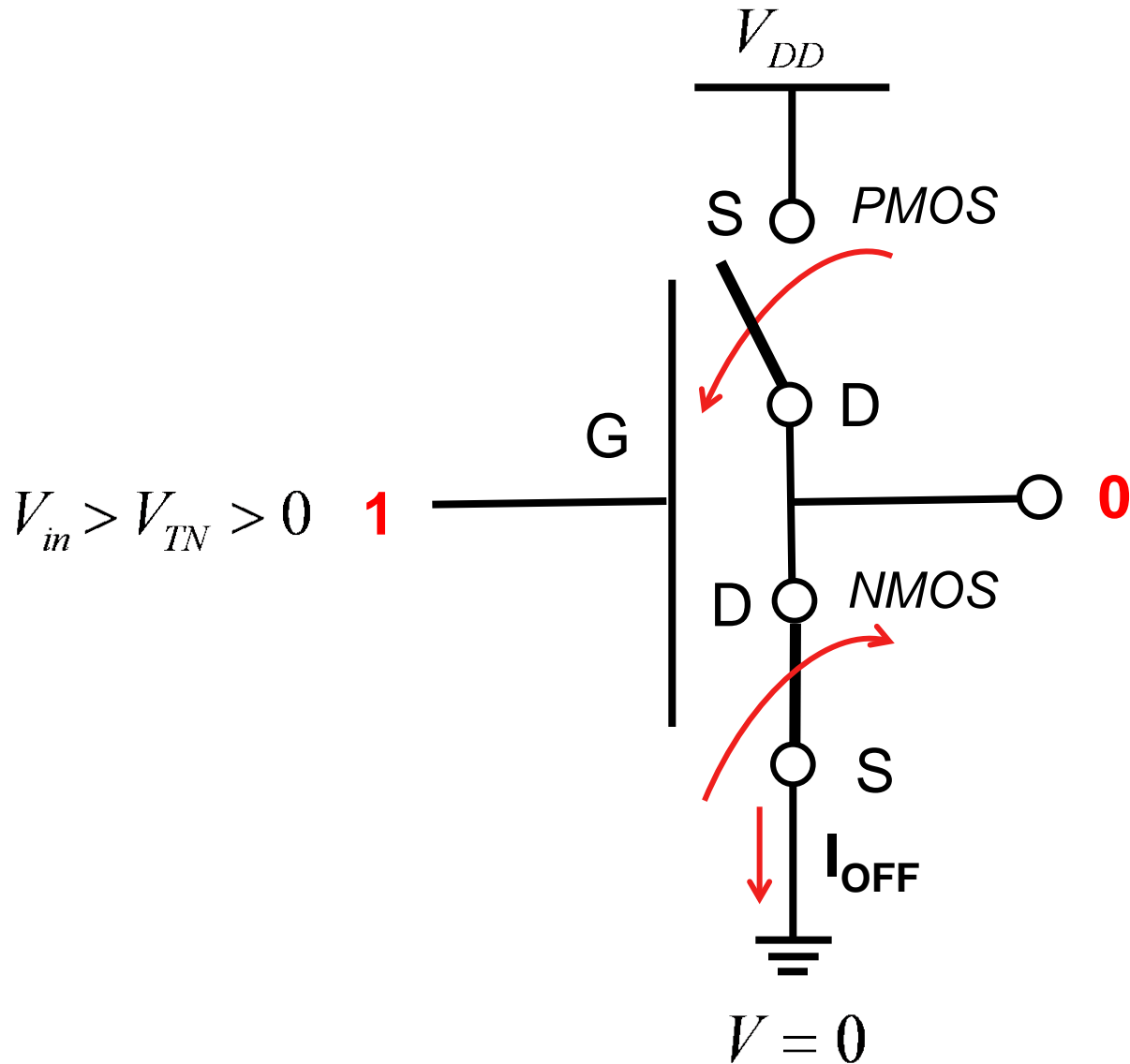


# CMOS inverter

 

# Two input NAND gate



AND		
A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

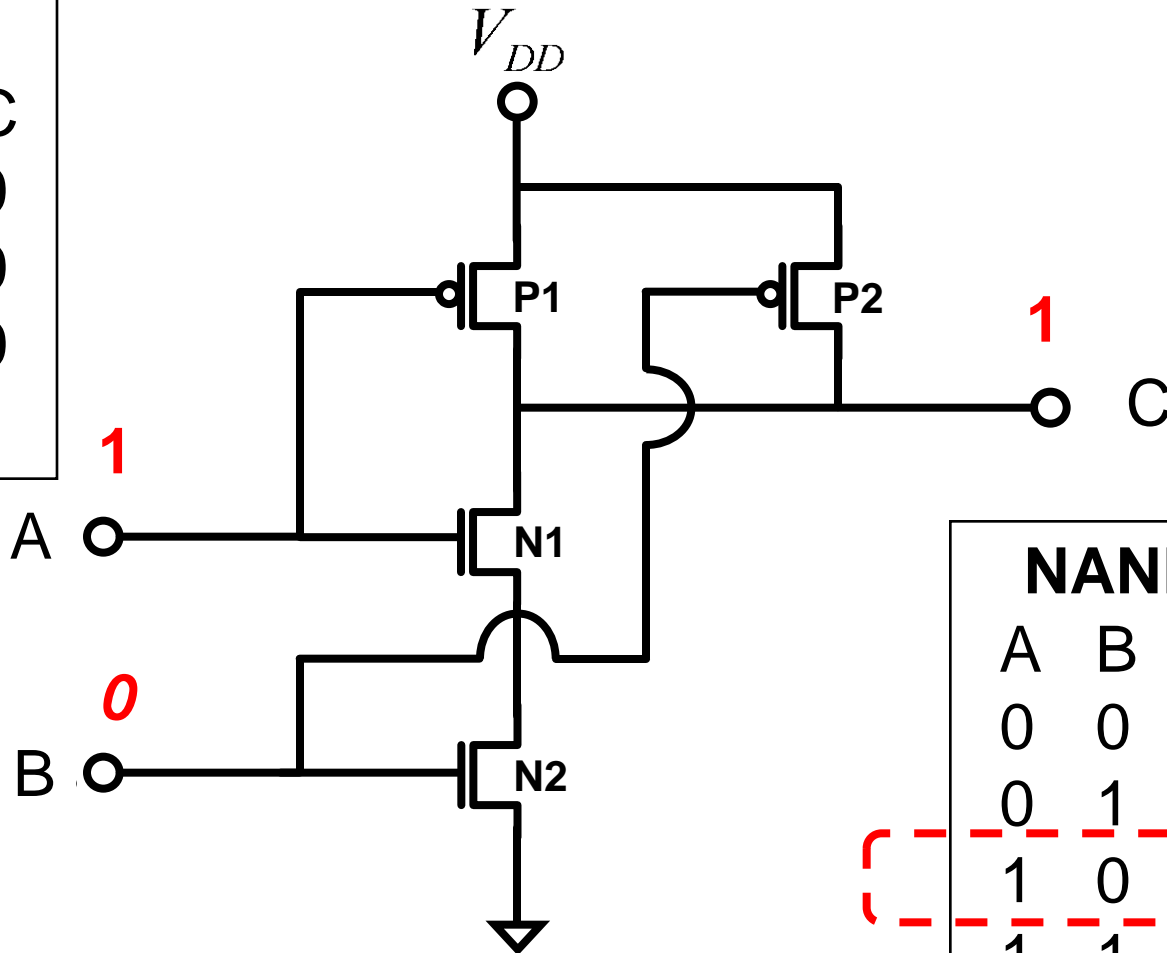


NAND		
A	B	C
0	0	1
0	1	1
1	0	1
1	1	0



# Transfer characteristics

  


# Gain restores signal levels

 

**noise margin**

# CMOS inverter

“pull up  
transistor”

 


“pull down  
transistor”


- 1) little current flows (power dissipation) unless switching
- 2) good noise margins if device has voltage gain

What determines *speed* and *power*?


## Switching (input 1 to 0)

 

# Switching (input 0 to 1)

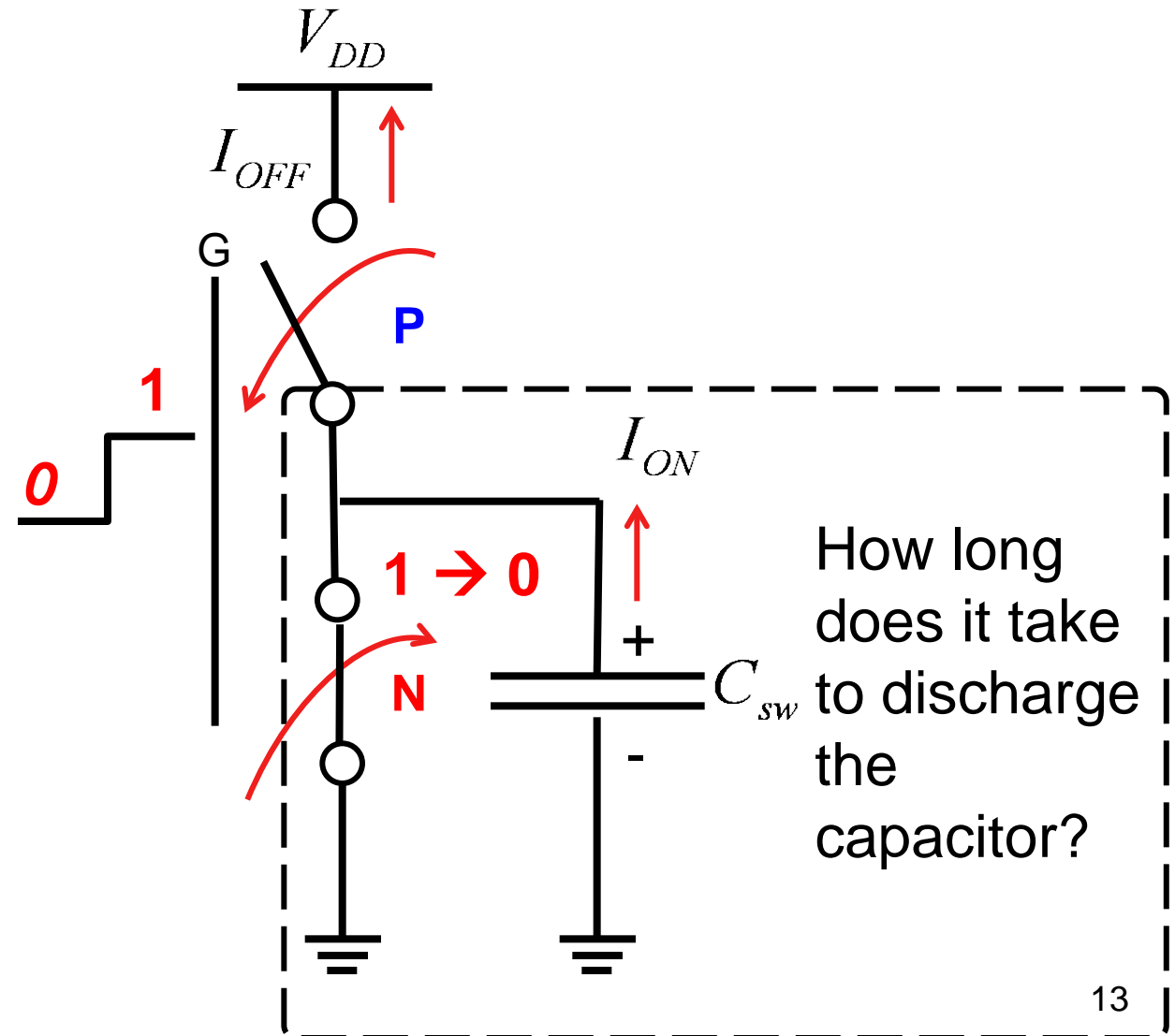

# Discharging time

 

$$Q = C_{sw} V_{DD}$$

$$I_{ON} = \frac{Q}{\tau}$$

$$\tau = \frac{C_{sw} V_{DD}}{I_{ON}}$$

**DC on-current controls  
switching time.**

# System speed

---

until ~1990:

device delay > interconnect delay

90 nm technology:

device delay: ~ 1ps

1 mm interconnect delay: ~ 6 ps

2015 (10 nm technology):


device delay: ~0.1ps

1 mm interconnect: ~30ps

J. Meindl, "Beyond Moore's law: the interconnect era," *Computing in Science and Engineering*, 2003

# Power dissipation

---

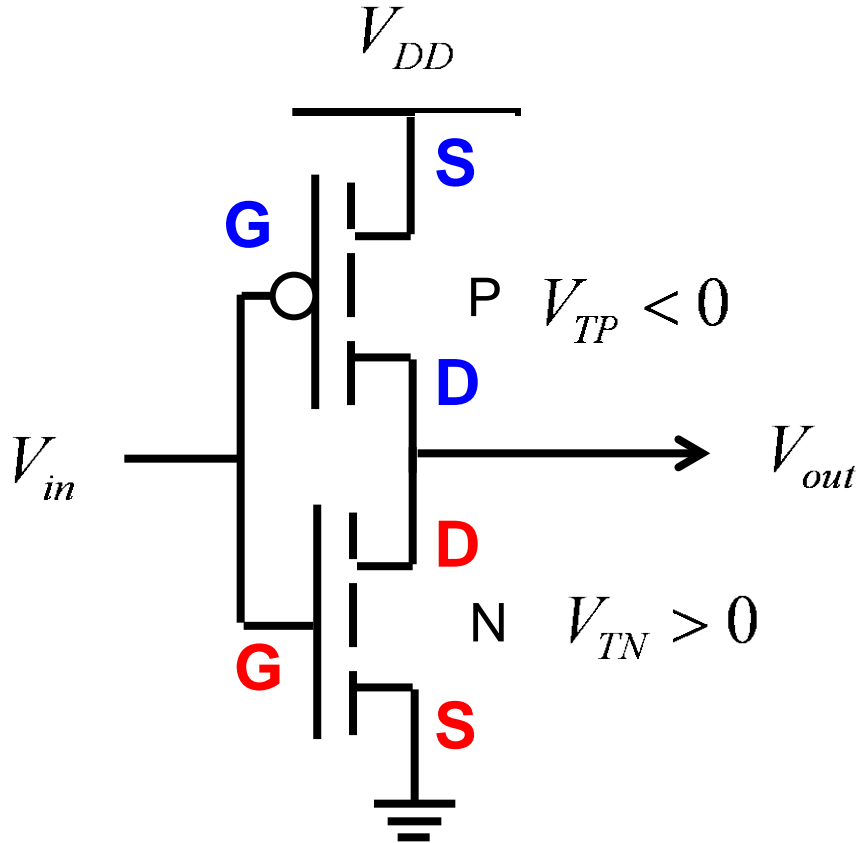


**Switching speed** is inversely proportional to the DC on-current.

The ideal CMOS inverter only dissipates power while switching (**dynamic power**).



Real CMOS also dissipates power when not switching (**static power**).



# Dynamic power

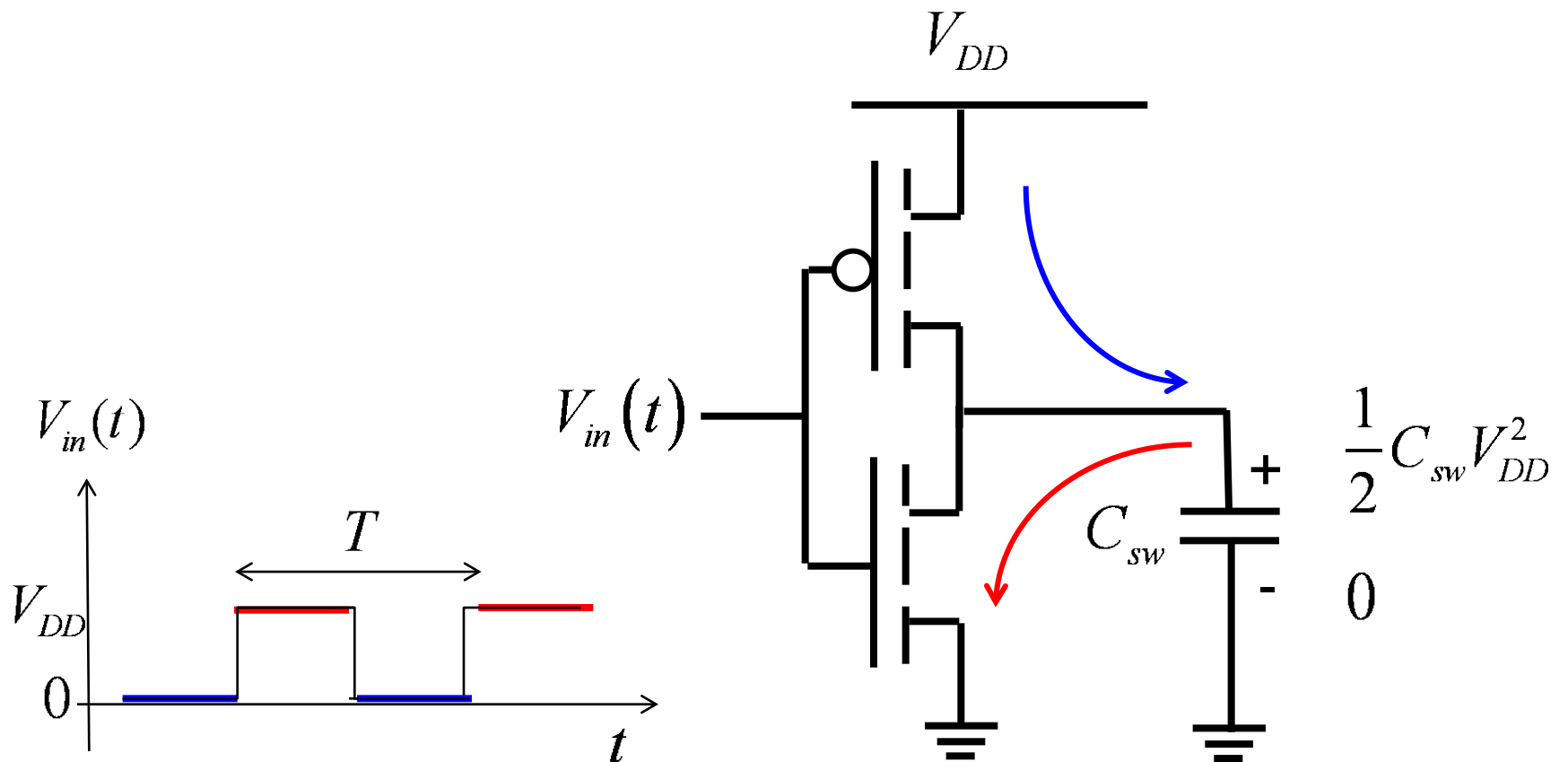

# Dynamic power

  

$$E_C(0) = \frac{1}{2} C_{sw} V_{DD}^2$$

$$E_C(T/2) = 0$$

$$P_{dynamic} = \frac{\Delta E}{T/2} = \frac{C_{sw} V_{DD}^2}{T} = f C_{sw} V_{DD}^2$$

$$P_{dynamic} = \alpha f C_{sw} V_{DD}^2$$

switching “activity”

# Dynamic power

---

$$P_{dynamic} = \alpha f C_{sw} V_{DD}^2$$


switching “activity”



At a given frequency, the dynamic power is proportional to **the power supply voltage squared** and to the **frequency**.

What determines the **static power**?

# Static power

 

$$P_{static} = I_{off} V_{DD}$$

$N_G$  = no. of gates

$$P_{static} = N_G I_{off} V_{DD}$$

# CMOS speed and power

---


$$\tau = C_{sw} V_{DD} / I_{ON}$$

$$P_{\text{dynamic}} = \alpha f C_{sw} V_{DD}^2$$

$$P_{\text{static}} = N_G I_{OFF} V_{DD}$$

- 1) Higher on-current means higher speed
- 2) Faster operation means more dynamic power
- 3) Lower  $V_{DD}$  means lower power
- 4) More leakage means more power dissipation

# Power constrained design

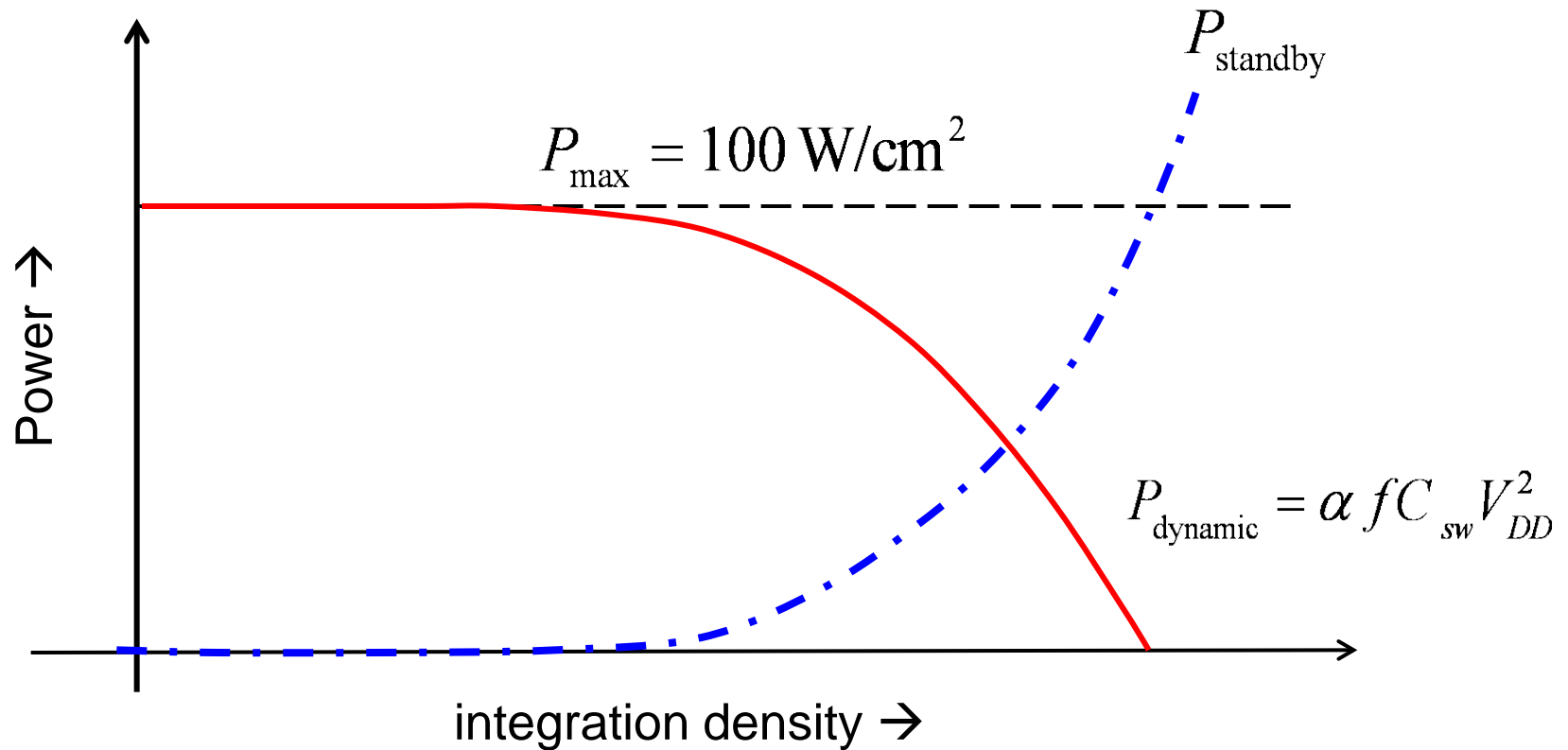

(after Dave Frank, IBM)

# Summary

---

Complementary MOS (CMOS) makes use of NMOS and PMOS transistors.

The basic building block of CMOS logic is the CMOS inverter.

Voltage gain is required for noise margins.

On-current, off-current, and power supply voltage are key parameters.

## Next topic: A primer on analog circuits

---

We now understand what's important for digital circuits. In the next lecture, we'll take a quick look **at analog and radio frequency** circuits.