

Essentials of MOSFETs

Unit 1: Transistors and Circuits


Lecture 1.3: Analog/RF Circuits

Mark Lundstrom


lundstro@purdue.edu
Electrical and Computer Engineering
Purdue University
West Lafayette, Indiana USA

Applications of MOSFETs


symbol

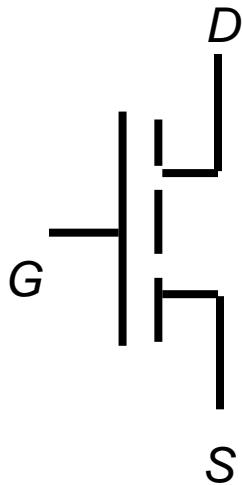

digital

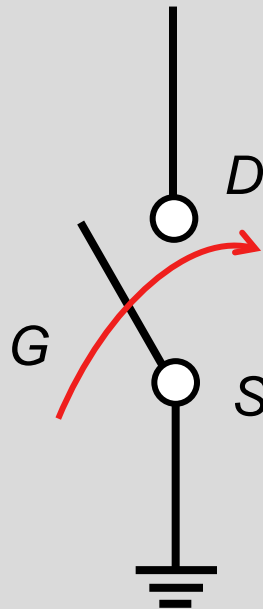

analog

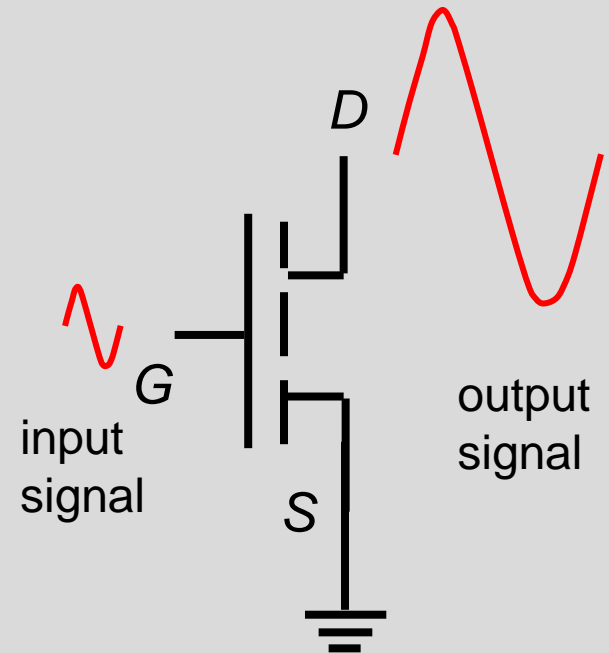

Why analog /RF? Why CMOS?


Many applications involve analog / RF signals:

- 1) many natural signals are analog (sensors)
- 2) disk drive electronics
- 3) wireless receivers and transmitters
- 4) optical receivers
- 5) microprocessors / memories

CMOS:

- 1) many systems are both analog and digital
- 2) CMOS dominant for digital electronics
- 3) CMOS performance is acceptable for many analog applications (but not, generally as good as bipolar)

Basic CS Amplifier

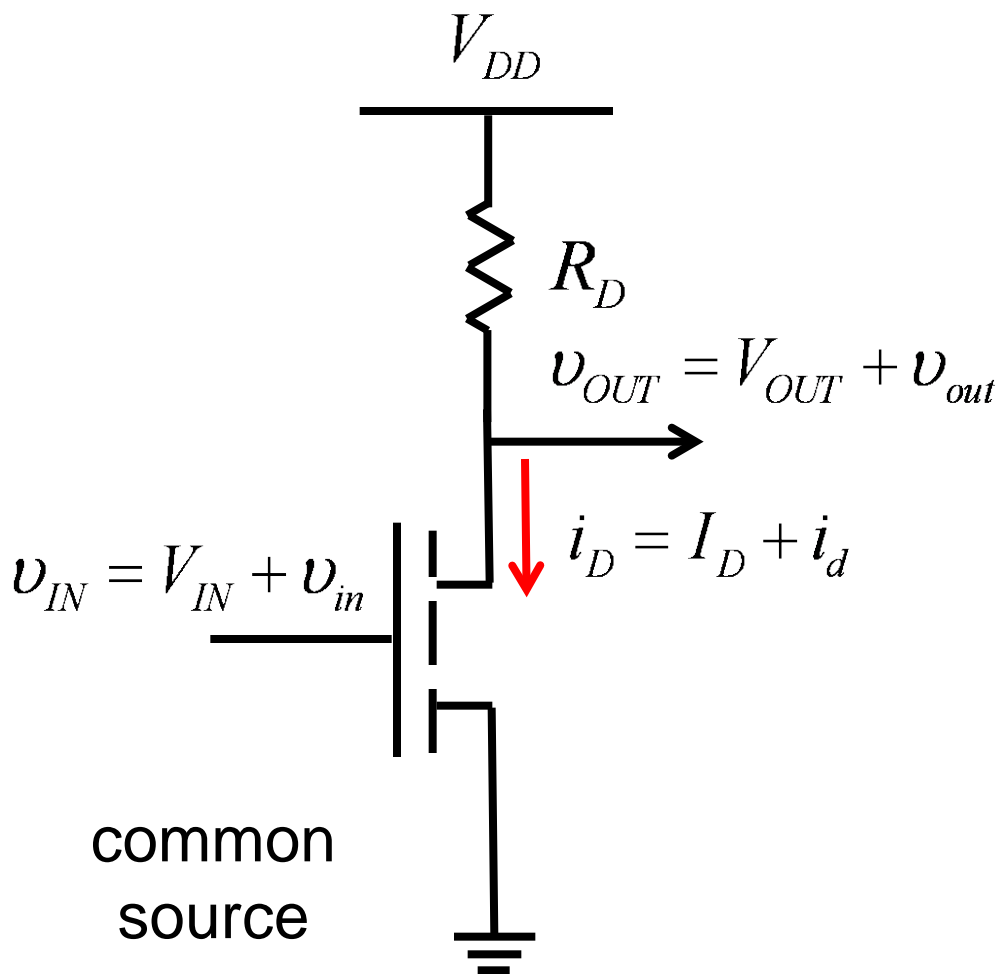

$$I_D = f(v_{GS}, v_{DS})$$


$$i_d = g_m v_{gs}$$

$$g_m = \frac{i_d}{v_{gs}} = \frac{\delta I_D}{\delta V_{GS}} \approx \left. \frac{\partial I_D}{\partial V_{GS}} \right|_{V_{DS}}$$

$$g_m \equiv \left. \frac{\partial I_D}{\partial V_{GS}} \right|_{V_{DS}}$$

Basic CS Amplifier: ac analysis

ac ground

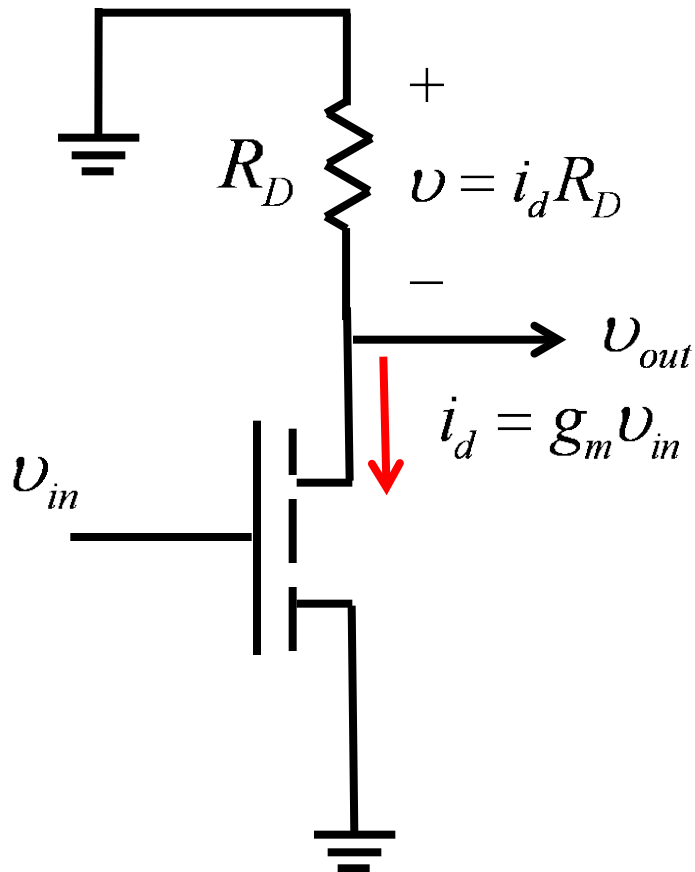


$$v_{out} = -i_d R_D = -g_m R_D v_{in}$$

$$A_v = \frac{v_{out}}{v_{in}} = -g_m R_D$$

Transconductance is an important analog figure of merit.

It is a measure of the transistor's ability to amplify.

Maximum gain

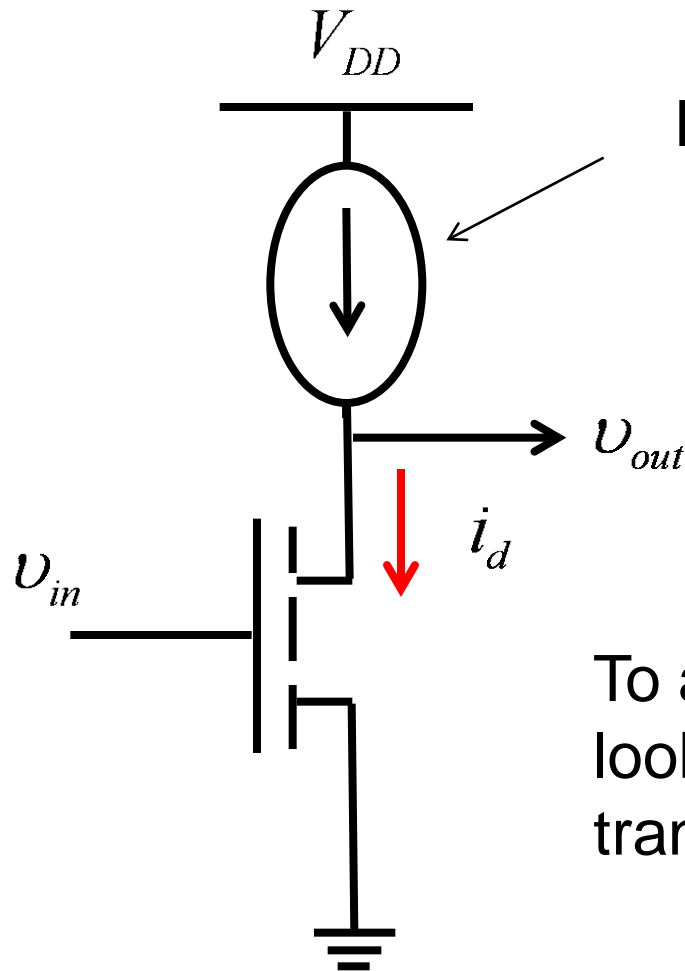


high impedance current source

$$R_D \rightarrow \infty$$

$$A_v(\text{max}) = ?$$


To answer this question, we need to look a little more carefully at the transistor.

Transconductance

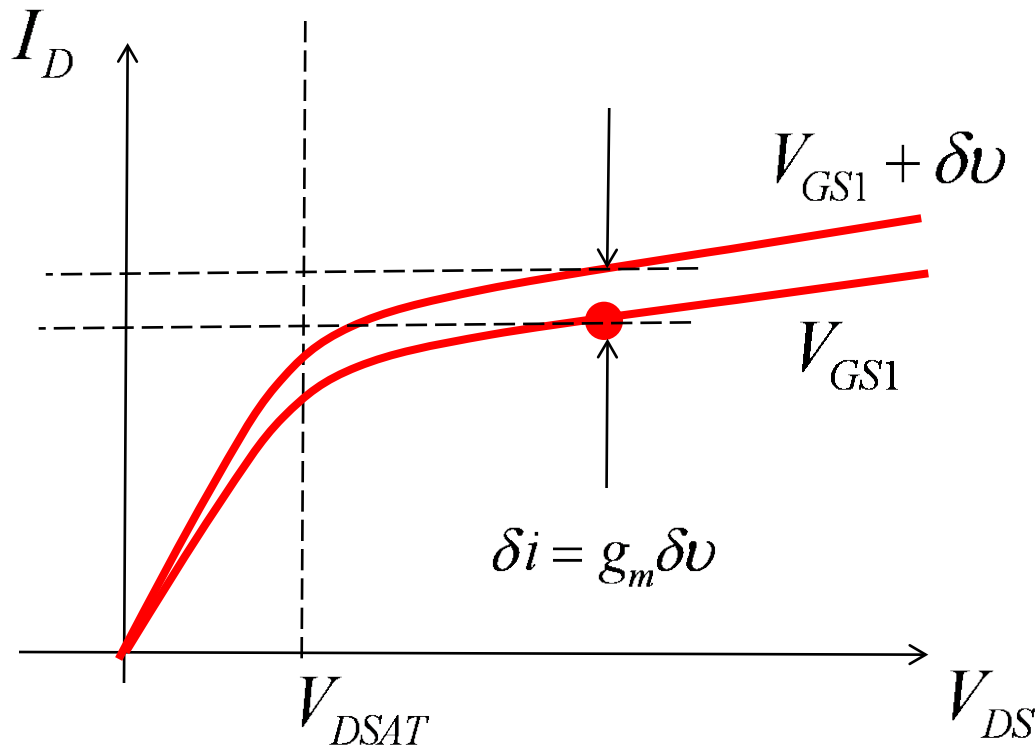

$$g_m \equiv \left. \frac{\partial I_D}{\partial V_{GS}} \right|_{V_{DS}}$$


Output resistance

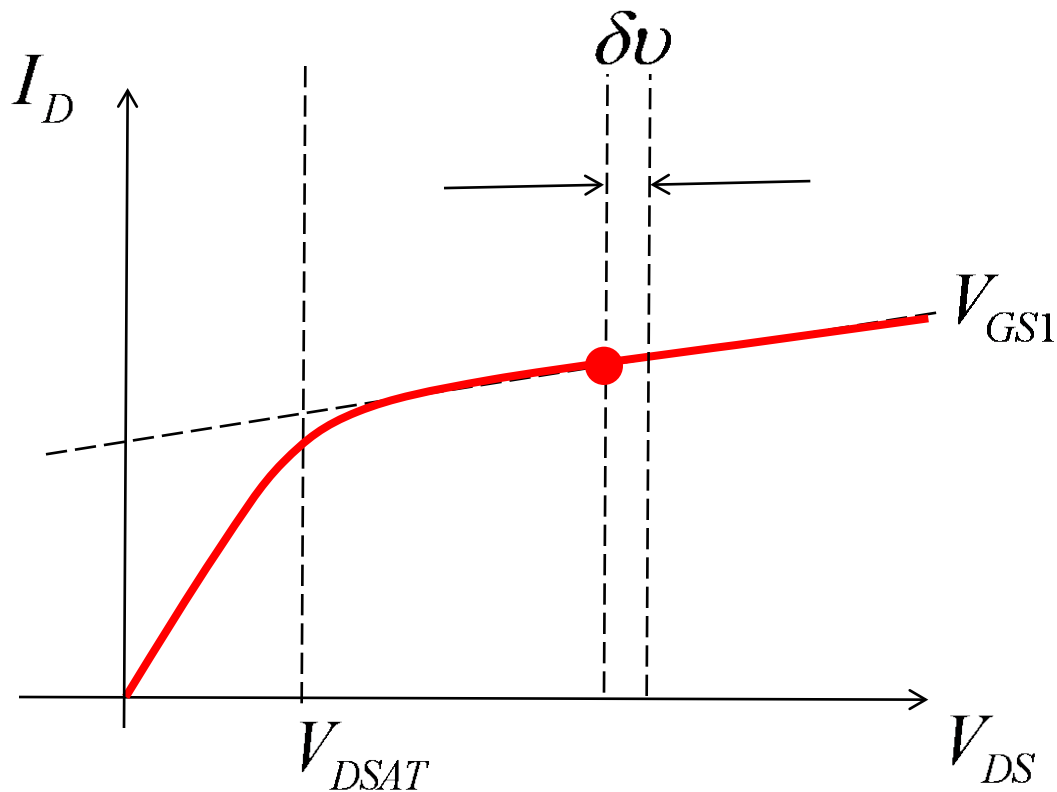

$$\delta i = \frac{\delta v}{r_o}$$

$$r_o \equiv \left[\partial I_D / \partial V_{DS} \big|_{V_{GS}} \right]^{-1}$$

Maximum gain

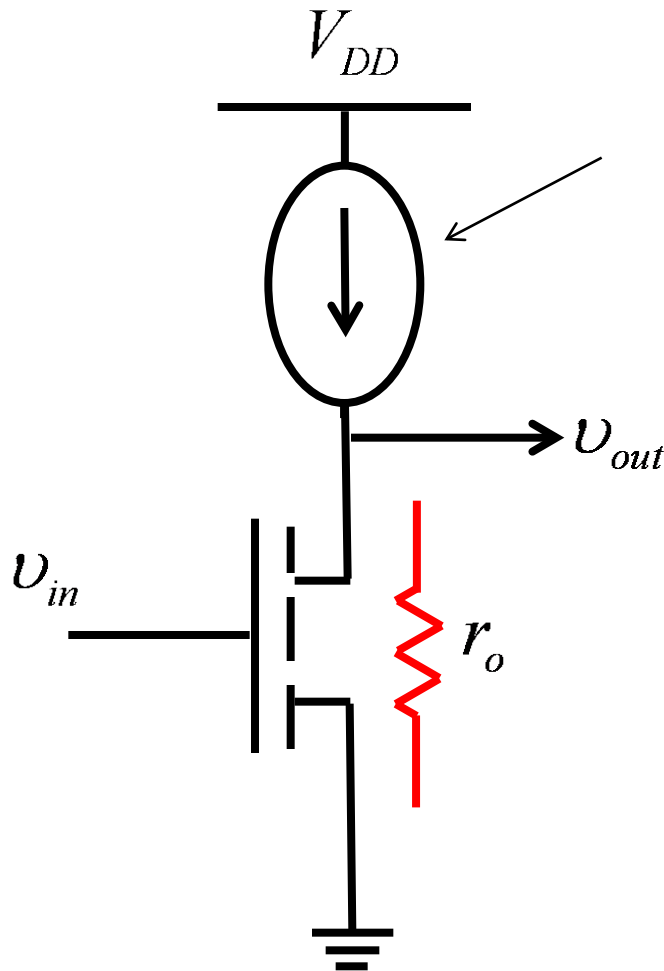


high impedance current source

$$A_v(\text{max}) = -g_m r_o$$

The **output resistance**, r_o , of the MOSFET is an important figure of merit.

So is the **self gain**, $g_m r_o$.

Self-gain for 65 nm digital CMOS

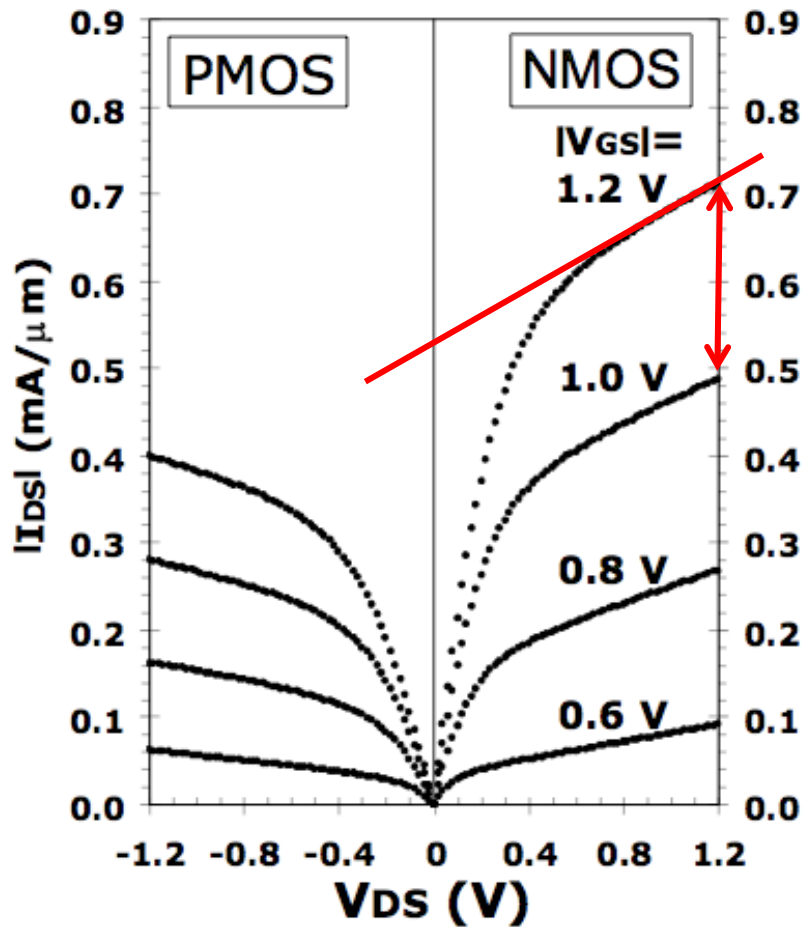

$$g_m \approx \frac{0.2 \text{ mA}/\mu\text{m}}{0.2 \text{ V}} = 1 \text{ mS}/\mu\text{m}$$


$$r_o \approx \frac{1.2 \text{ V}}{0.18 \text{ mA}/\mu\text{m}} \approx 7 \text{ K}\Omega\text{-}\mu\text{m}$$

$$|A_v(\text{max})| = g_m r_o \approx 7$$

C.-H. Jan. et al., 2005 IEDM

Lundstrom: 2018



Self-gain vs. scaling

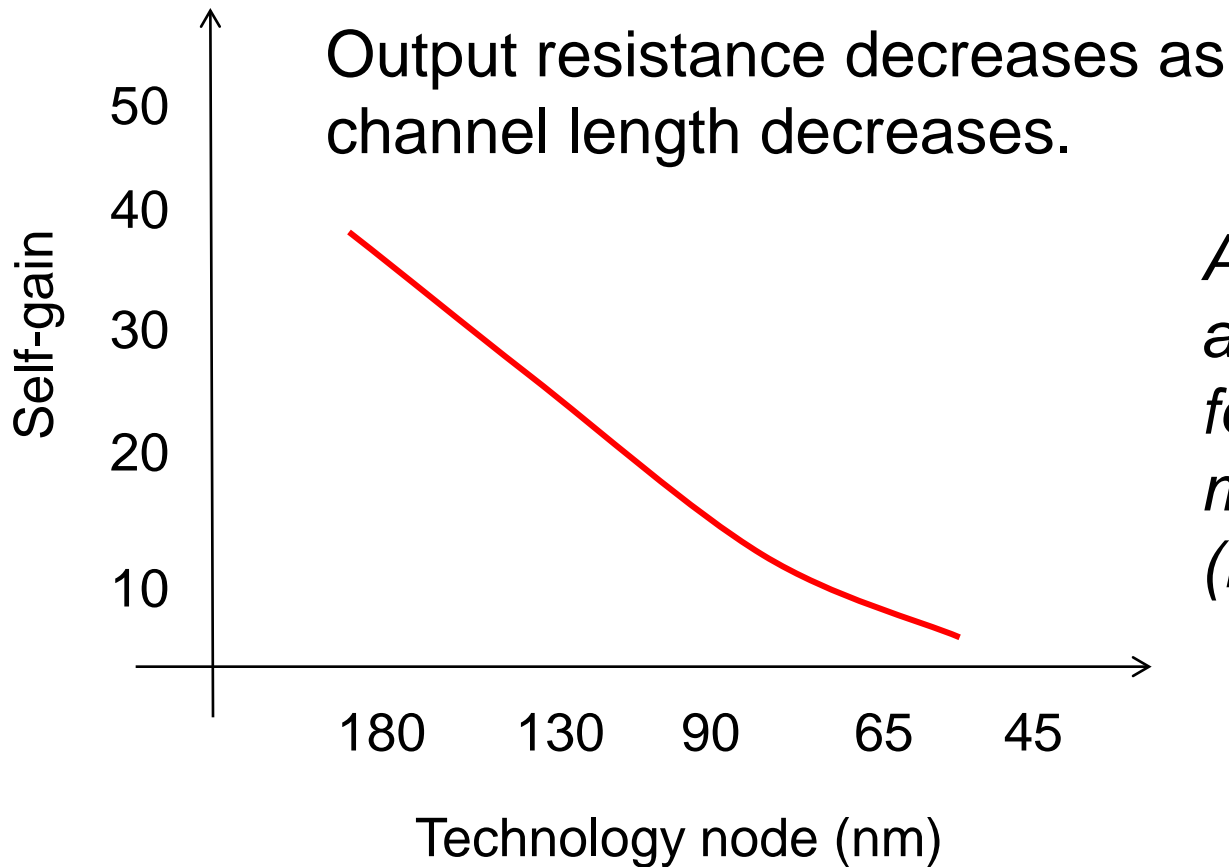

Analog designers are frequently forced to use non-minimum length (NML) devices.

High frequency performance

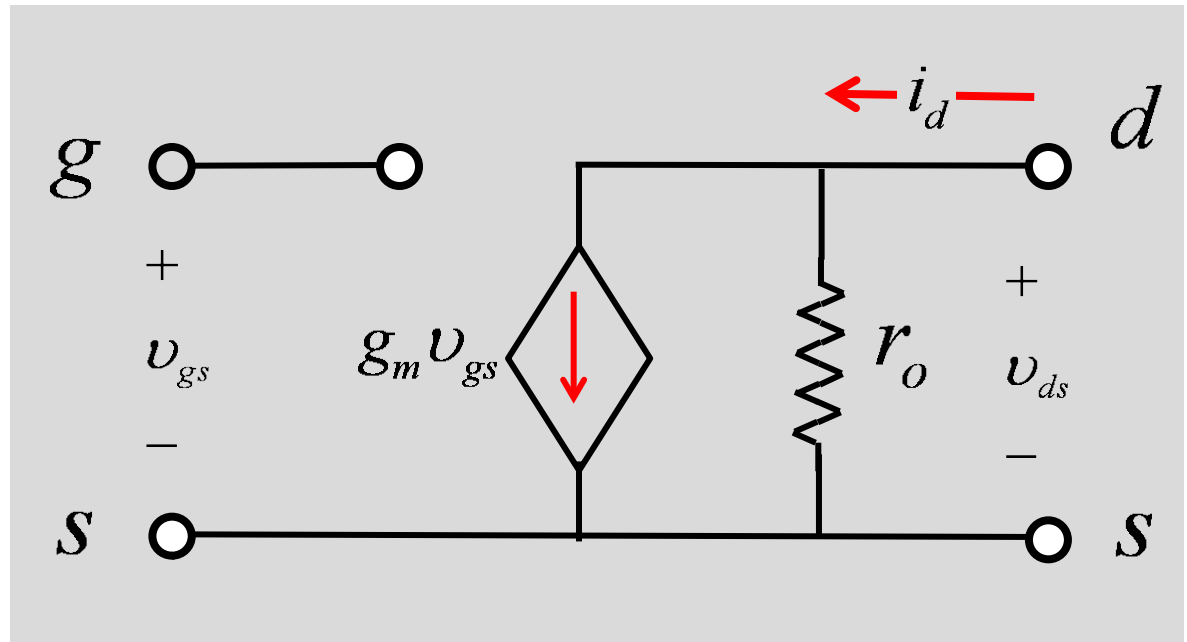
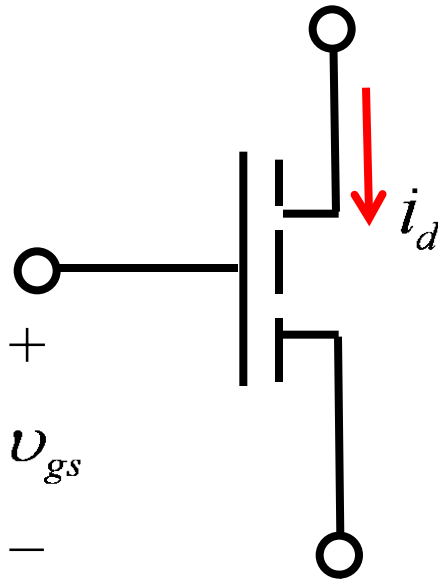
Small-signal, **low frequency** equivalent circuit



$$i_d = g_m v_{gs} + v_{ds} / r_o$$


High frequency performance

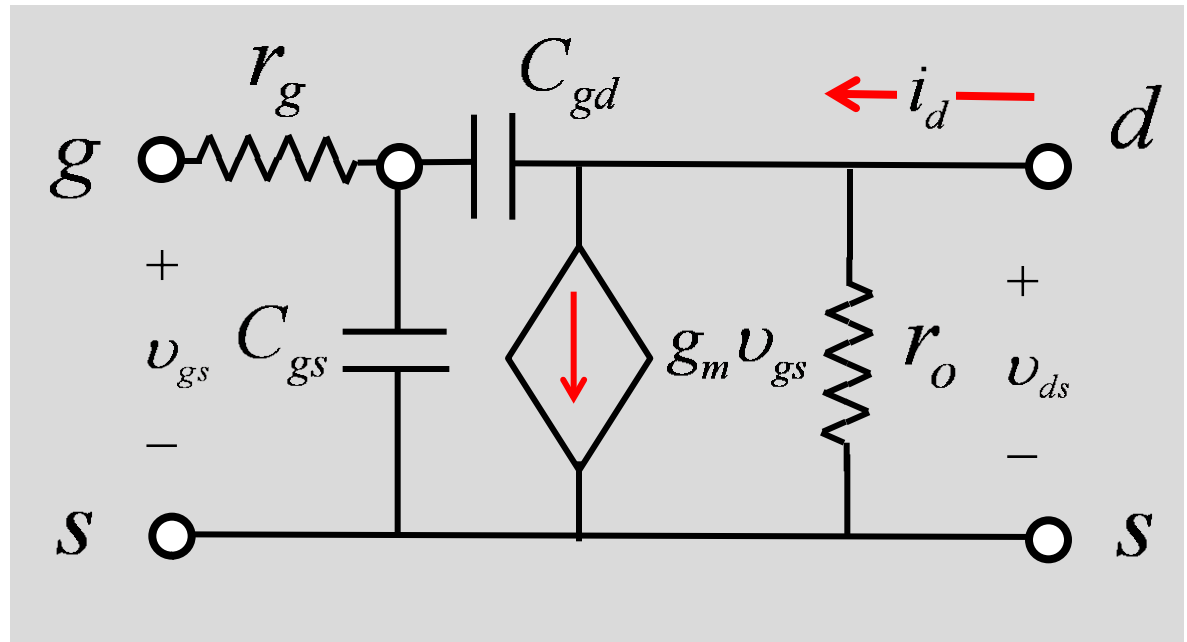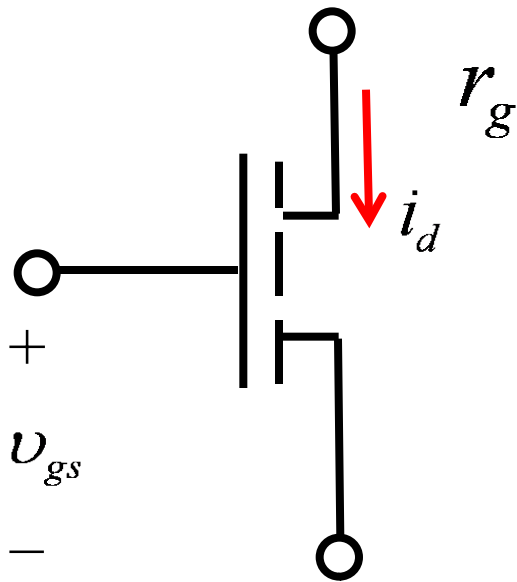Small-signal, **high frequency** equivalent circuit



$$i_d = g_m v_{gs} + v_{ds} / r_o$$

Short circuit current gain

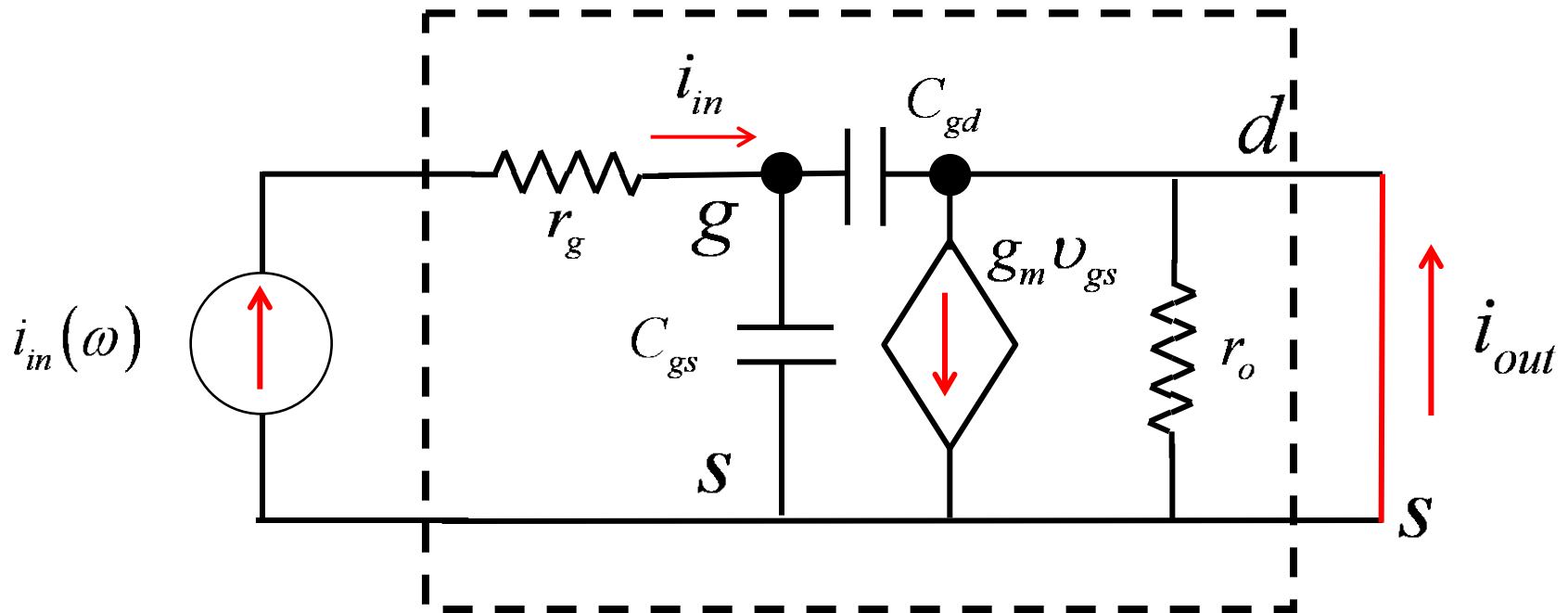

$$\left. \begin{aligned} i_{out} + (j\omega C_{gd})v_{gs} &= g_m v_{gs} \rightarrow i_{out} \approx g_m v_{gs} \\ v_{gs} &= i_{in} \frac{1}{j\omega(C_{gs} + C_{gd})} \end{aligned} \right\}$$

$$i_{out} \approx \frac{g_m}{j\omega C_{TOT}} i_{in}$$


Gain-bandwidth product

$$i_{out} \approx \frac{g_m}{j\omega C_{TOT}} i_{in}$$

$$|\beta(\omega)| \approx \frac{g_m}{\omega C_{TOT}}$$

$$|\beta(\omega_T)| = 1 = \frac{g_m}{\omega_T C_{TOT}}$$
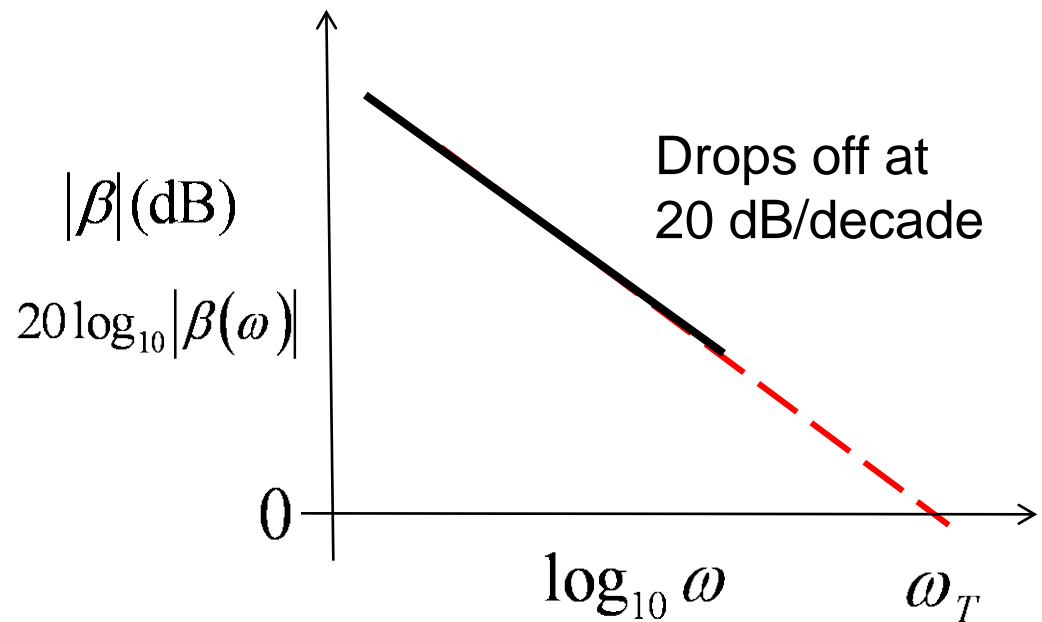
$$\omega_T = \frac{g_m}{C_{TOT}} = 2\pi f_T$$



Gain-bandwidth product

$$\omega_T = 2\pi f_T = \frac{g_m}{C_{TOT}}$$

The **gain-bandwidth product** is an important figure of merit for high frequency transistors.

$$f_{MAX}$$

$$f_T = \frac{g_m}{2\pi C_{TOT}}$$

insensitive to r_g and r_o

independent of W

channel length scaling
increases f_T

$$f_{MAX} \approx \frac{\omega_T}{\sqrt{4r_g \left(1/r_o + \omega_T C_{gd} \right)}}$$

sensitive to
parasitics

- r_g
- r_o
- C_{gd}

Another figure of merit is f_{MAX} , the ***maximum frequency of oscillation*** or the ***unity power gain***.

Analog figures of merit

transconductance

device noise


self gain

device mismatch

f_T and f_{MAX}

device linearity

Source coupled pairs

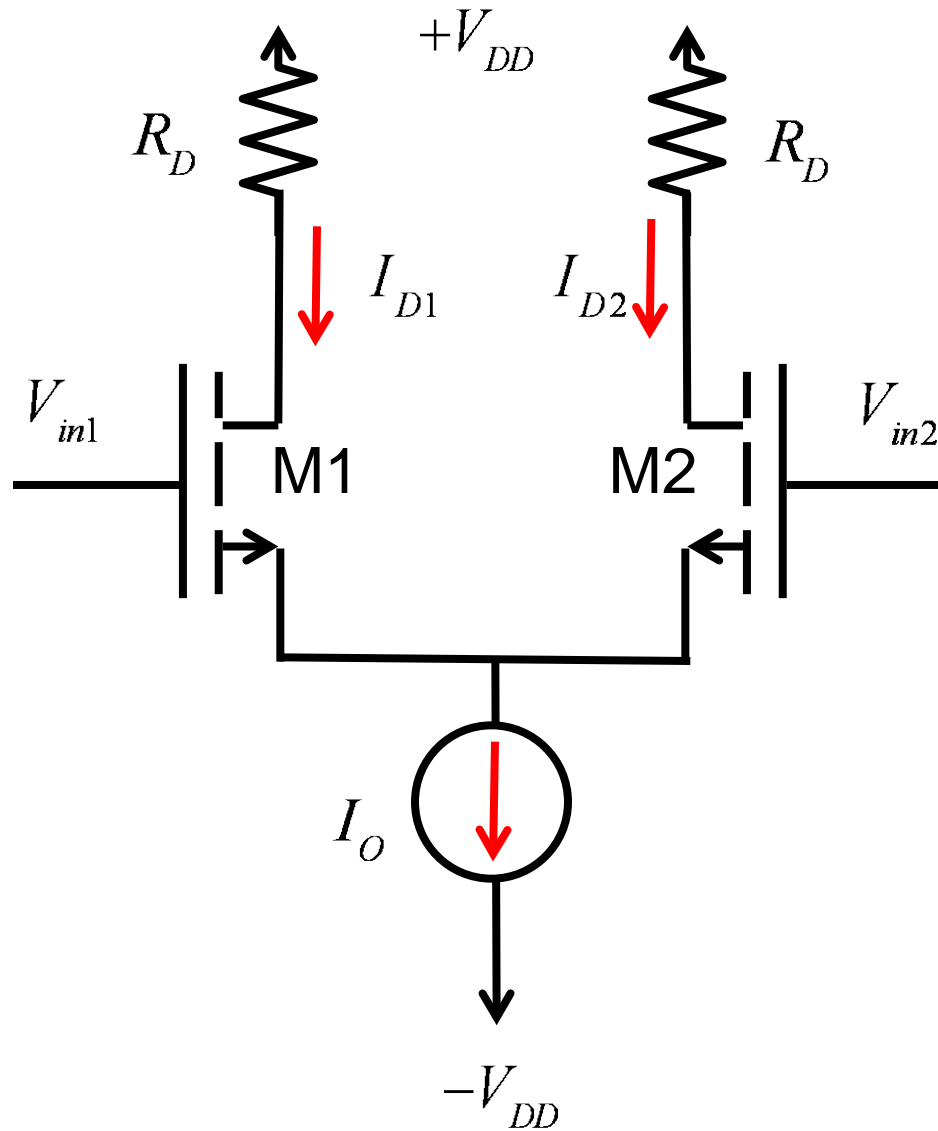

Summary

Small signal transconductance is an important figure of merit for a transistor.

Self-gain ($g_m r_o$) is another important figure of merit.

f_T and f_{max} are key figure of merit for RF applications.

Other important device parameters are noise, mismatch, and linearity.

Next topic: Device metrics

Now that we understand what's important for digital and analog circuits, we can define an easily-measured, relevant set of **device metrics**.