

Essentials of MOSFETs


Unit 5: Additional Topics

Lecture 5.2: Power MOSFETs

Mark Lundstrom

lundstro@purdue.edu
Electrical and Computer Engineering
Purdue University
West Lafayette, Indiana USA

Power MOSFETs are used as switches

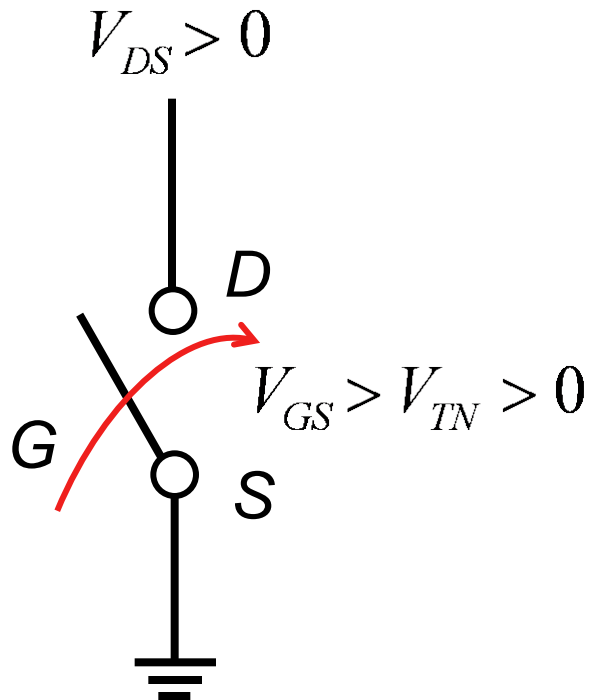


When **on**, the resistance of the switch should be as low as possible.

When **off**, the device should block current to as high a voltage as possible.

- 1) Low on resistance
- 2) High breakdown voltage

Applications

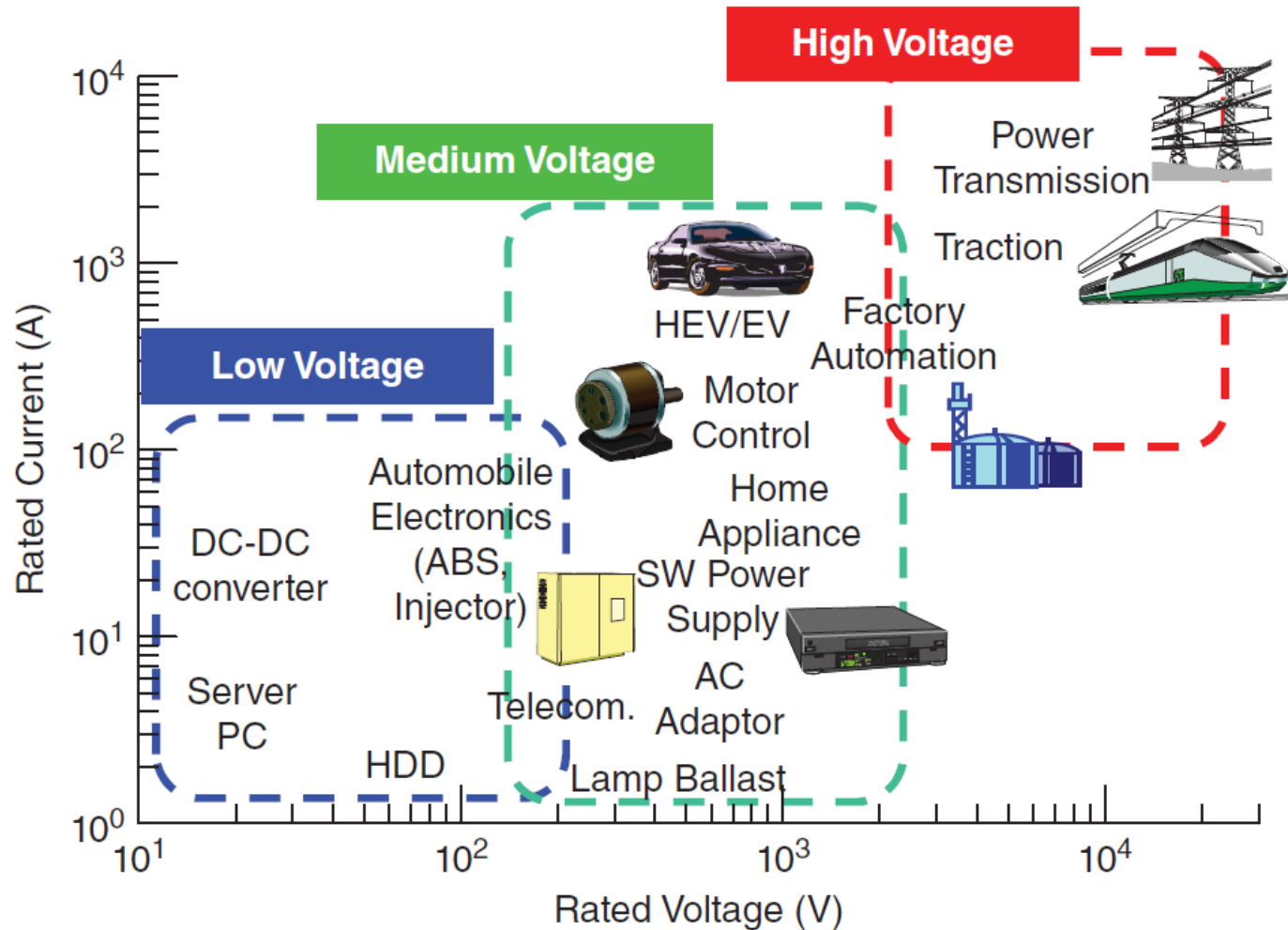

T. Kimoto and J. A. Cooper, *Fundamentals of Silicon Carbide Technology*, Wiley (2014).


Power semiconductor devices

There are several different types of three-terminal, power semiconductor switching devices – e.g.

- Vertical Diffused MOS transistors (DMOSFET)
- V-groove trench MOSFETs
- Trench MOSFETs
- Insulated Gate Bipolar Transistors (IGBT)
- Superjunction devices

To illustrate some of the considerations, we will only discuss the DMOSFET transistor.

On and off-states

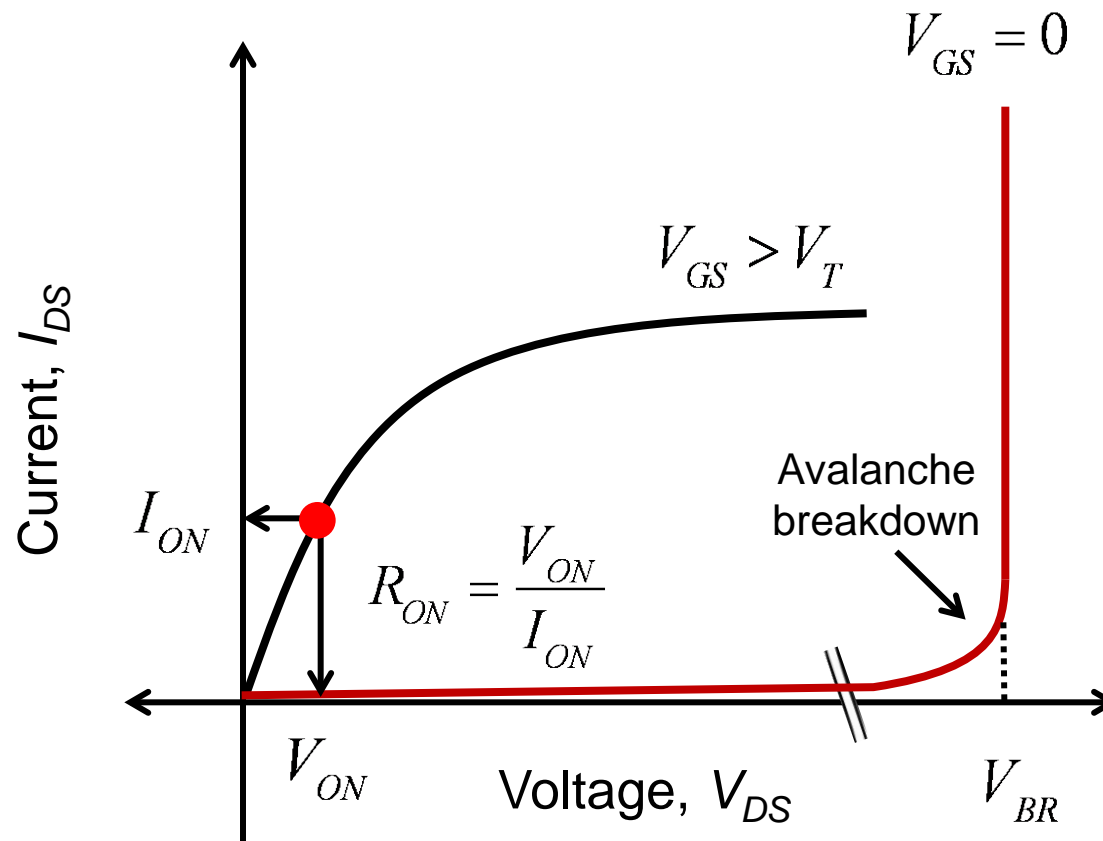

Device design goals

On-state: Maximize I_{ON} (minimize R_{ON})

Off-state: Maximize V_{BR}

Minimize area


Specific on-resistance: $R_{ON,SP} = R_{ON} \times A$

Device design goals

High currents require large W (MOSFET width)

High breakdown voltage requires that we spread the voltage drop out (long channels) to minimize the electric field.

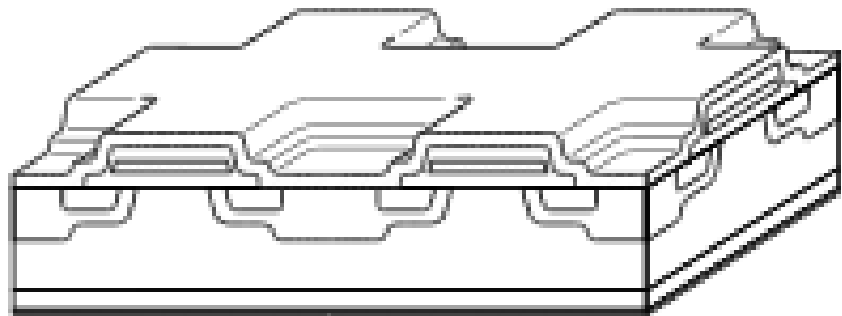To achieve these goals, power MOSFETs use vertical current flow and cellular structures.




https://en.wikipedia.org/wiki/Power_MOSFET

Area must be minimized

$$R = \rho \frac{L}{A} \quad R \times A = R_{SP} = \rho L \Omega - \text{cm}^2 \quad \text{specific resistance}$$

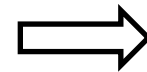
$$A_{DIE}(\text{cm}^2) = \frac{R_{ON,SP}(\Omega - \text{cm}^2)}{R_{ON}(\Omega)}$$




Die cost




DMOSFET

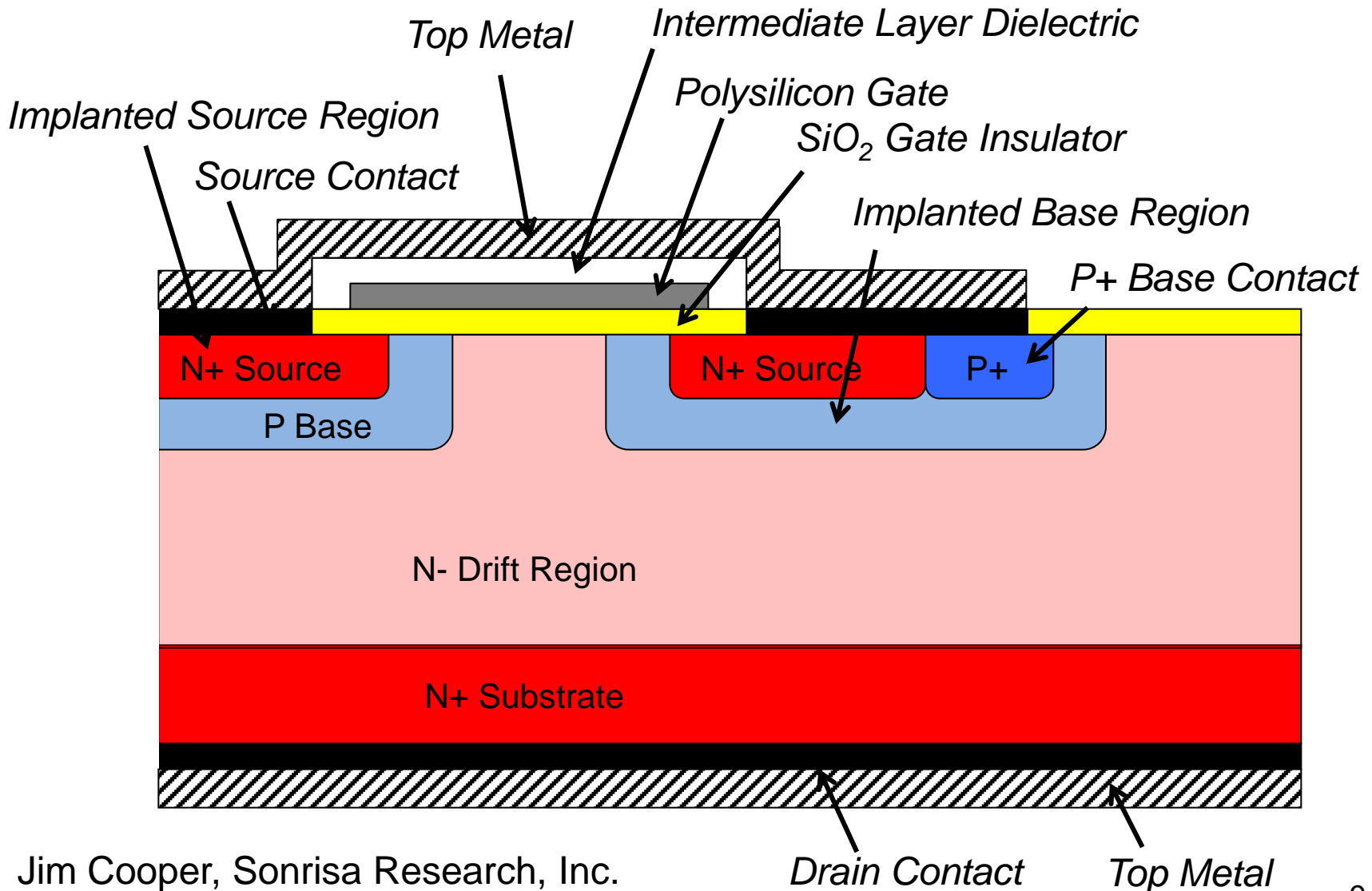

DMOSFET: On-state

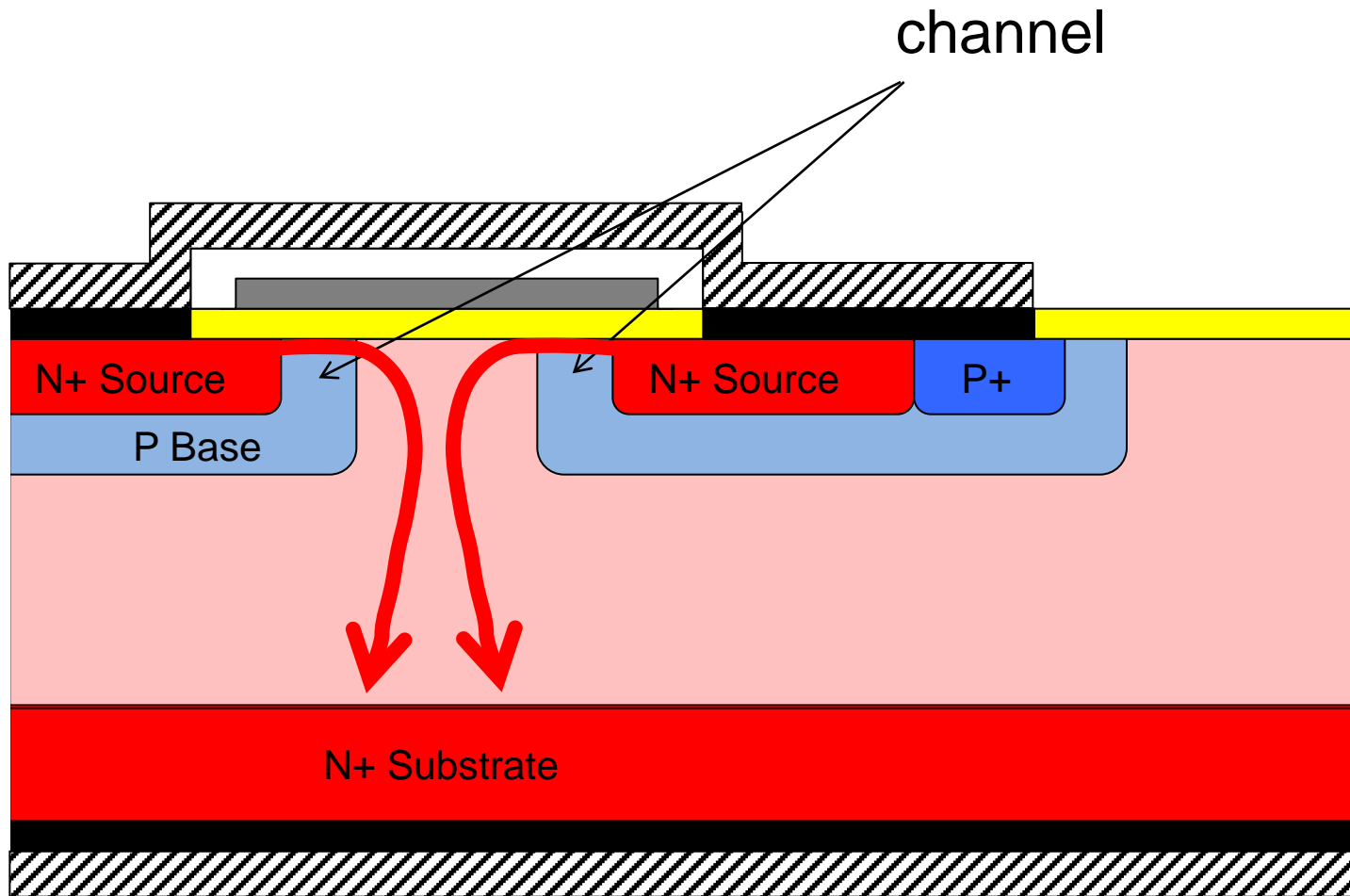

DMOSFET: On-state resistances

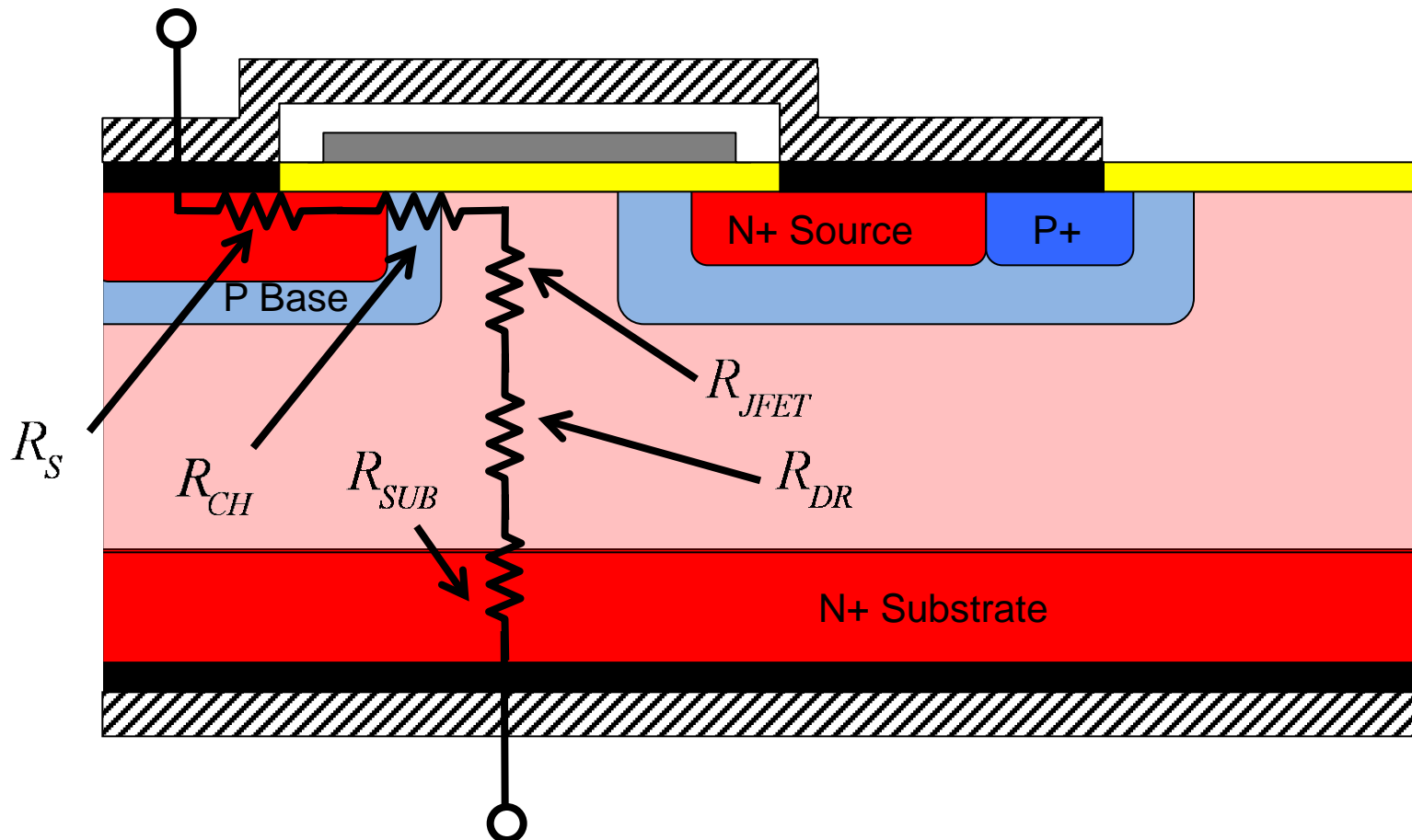

On resistance

$$R_{ON} = R_S + R_{CH} + R_{JFET} + R_{DR} + R_{SUB}$$


For high voltage MOSFETs, the N^- region is thick, so R_{DR} dominates.

$$R = \rho \frac{t_{DR}}{A}$$


$$R_{DR,SP} = \frac{1}{N_{DR} q \mu_{DR}} t_{DR} \left(\Omega - \text{cm}^2 \right)$$

$$R \times A = R_{SP} = \rho t_{DR} \Omega - \text{cm}^2$$


DMOSFET: On resistance

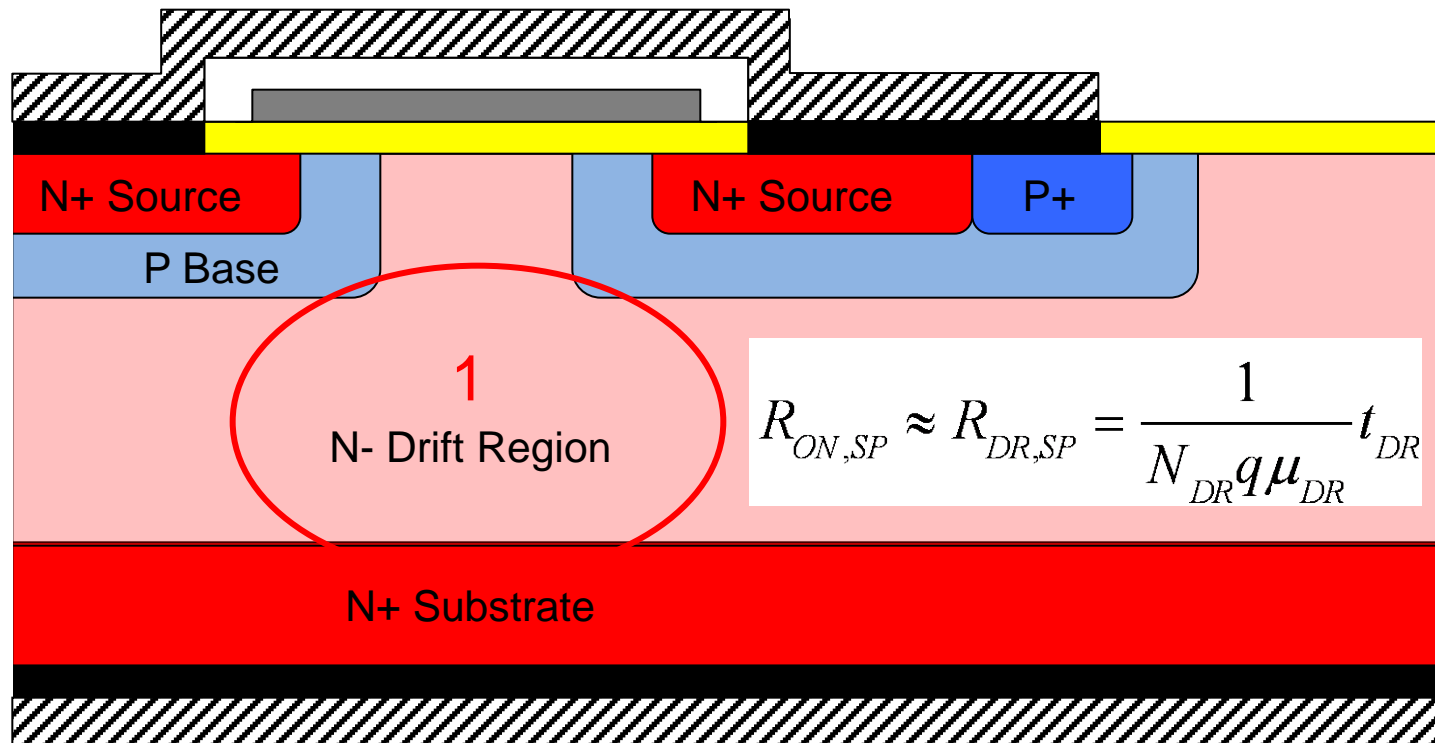

DMOSFET: Breakdown voltage

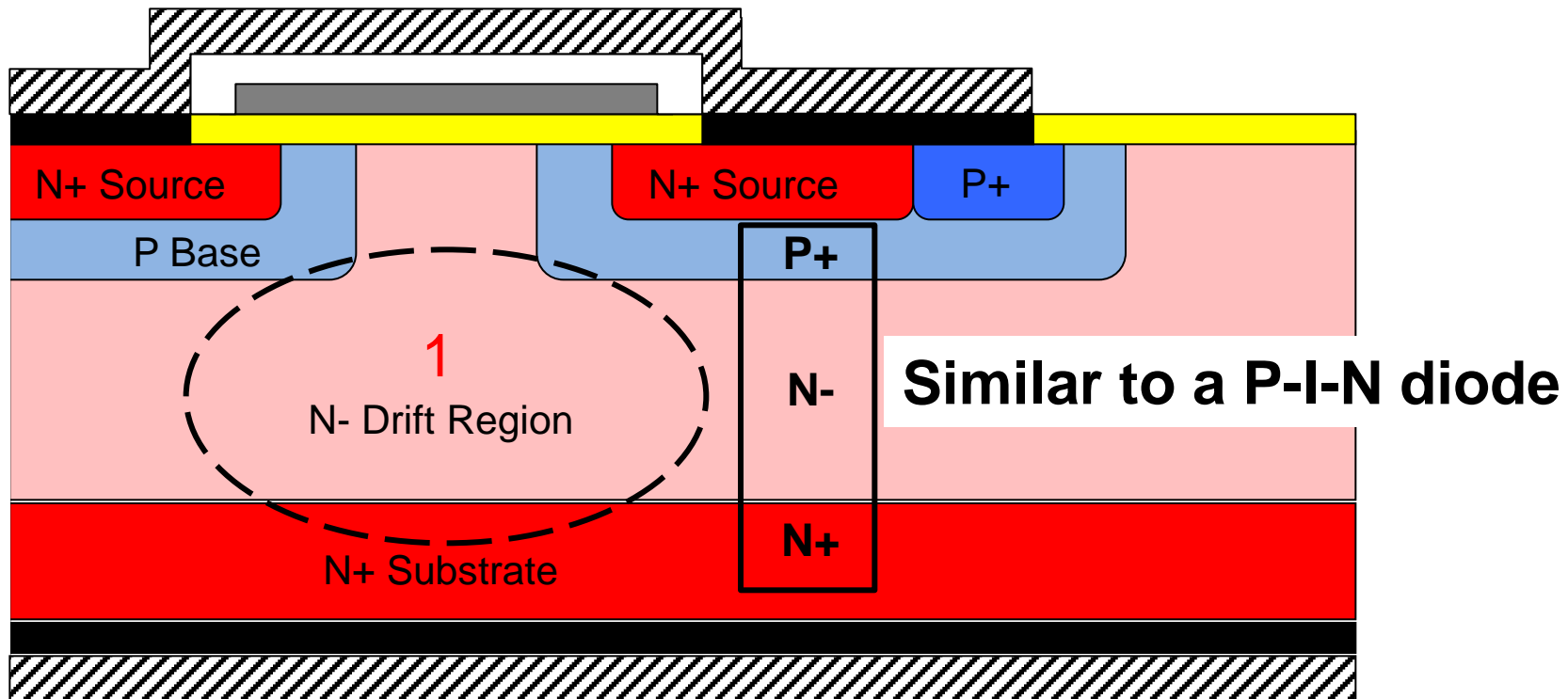


P+/N- diode at reverse breakdown

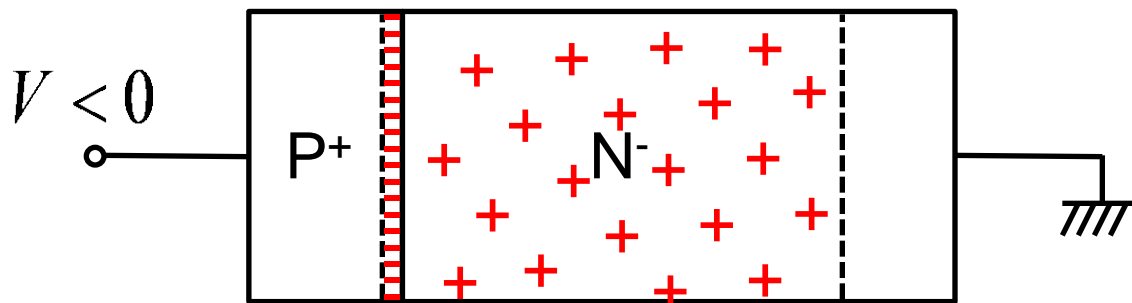


For a one-sided step junction,
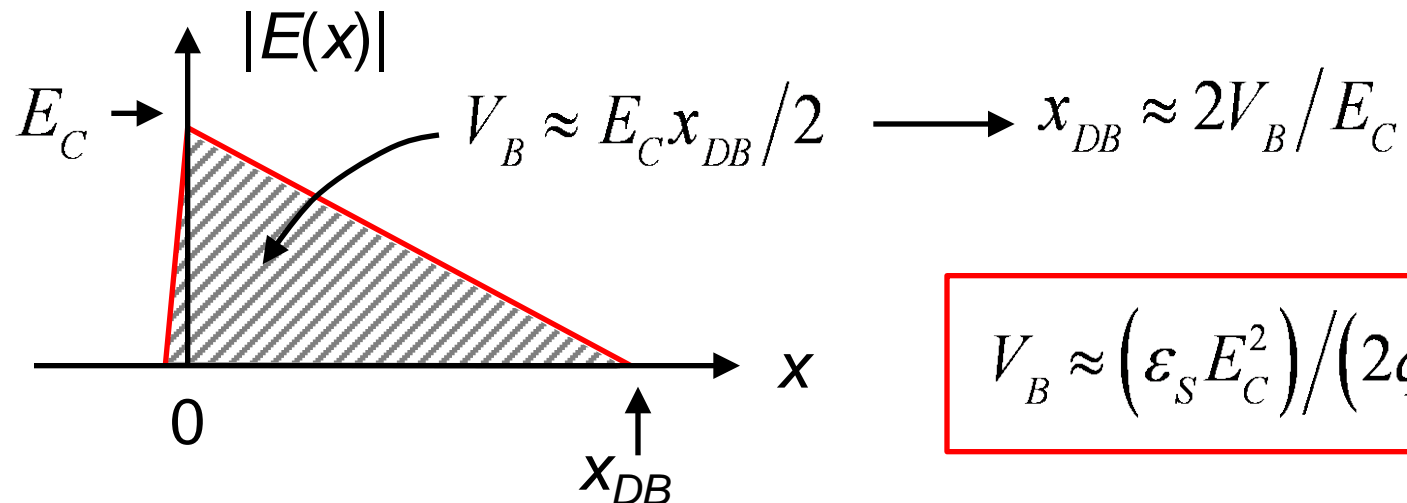
$$x_{DB} \approx \sqrt{2\epsilon_S V_B / (qN_D)}$$




$$V_B \approx (\epsilon_S E_C^2) / (2qN_D)$$

P+/N- diode at reverse breakdown

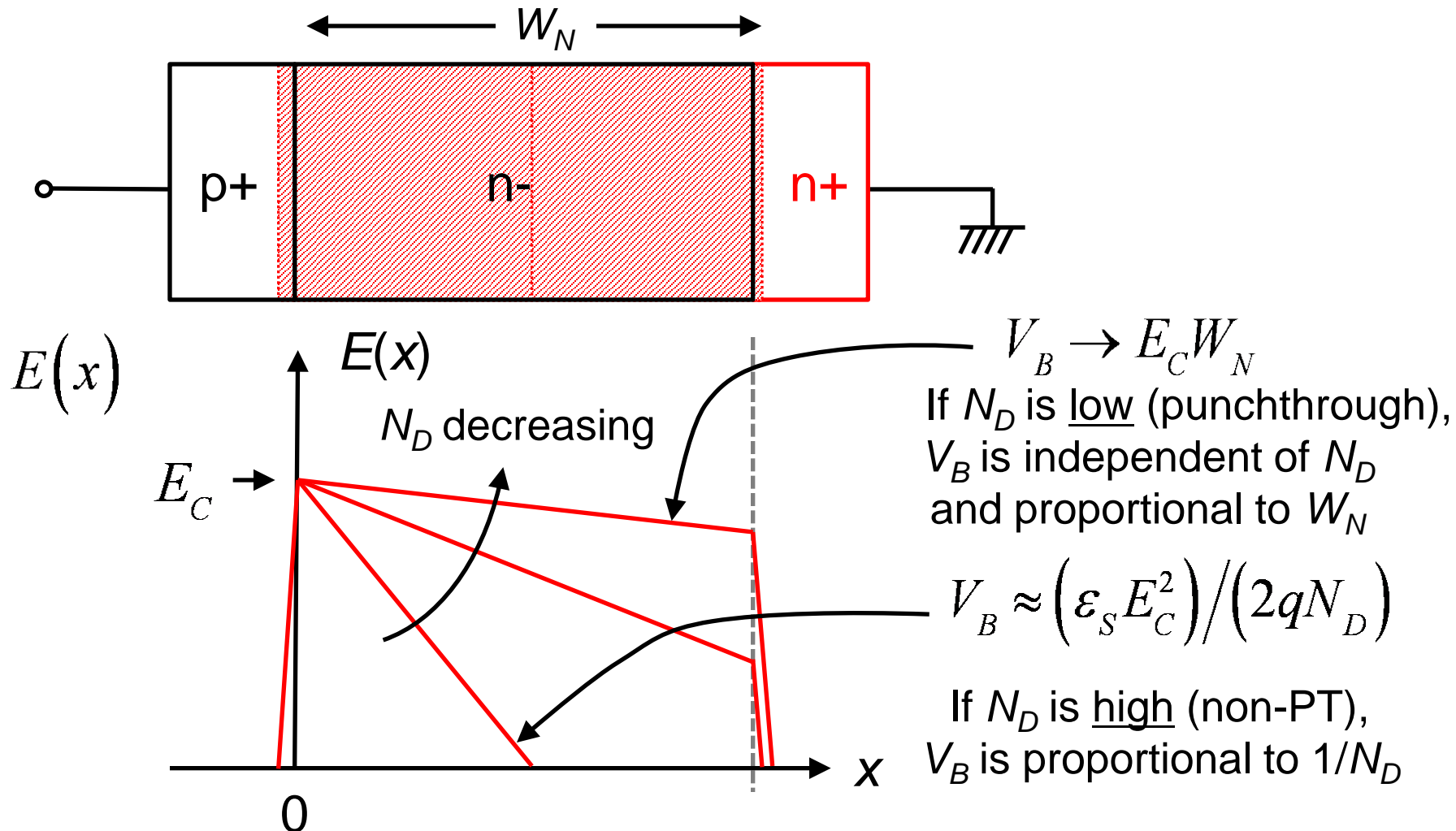

Specific on-resistance

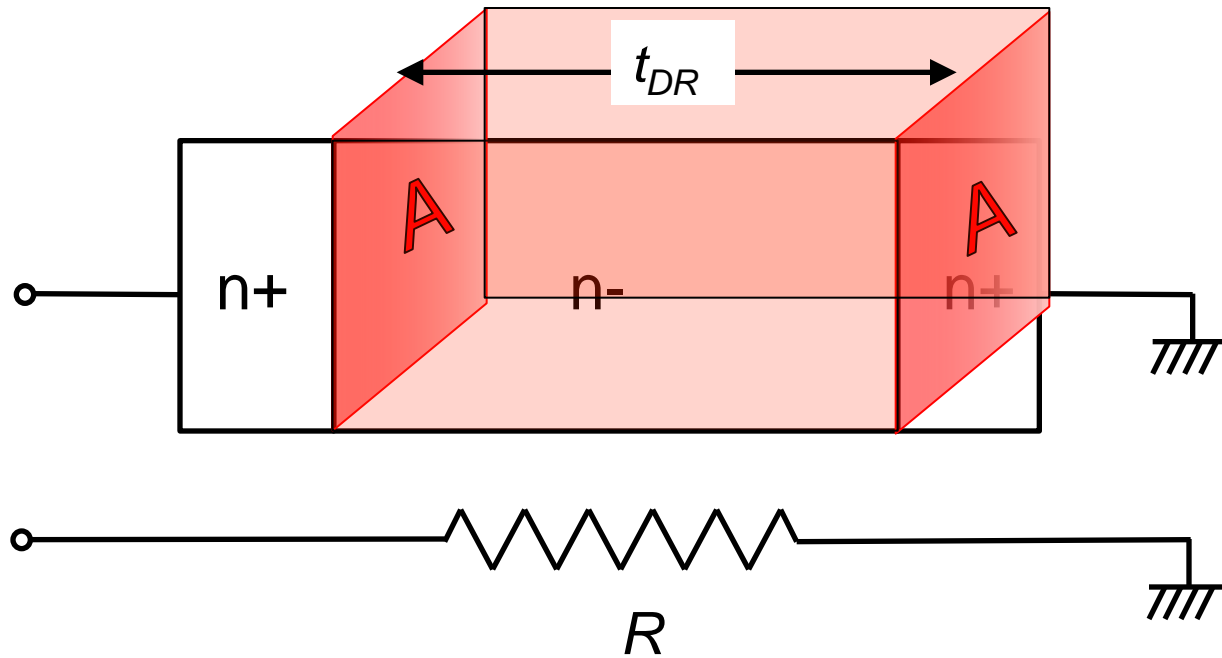

$$R_{ON,SP} = R \times A = \left(\rho \frac{t_{DR}}{A} \right) A = \frac{t_{DR}}{q\mu_n N_D}$$


Resistance – breakdown voltage trade-off

$$V_B \approx (\epsilon_S E_C^2) / (2qN_D) \quad \Rightarrow \quad N_D = (\epsilon_S E_C^2) / (2qV_B)$$


$$V_B = E_C x_{DB} / 2 \quad \Rightarrow \quad x_{DB} = 2V_B / E_C = t_{DR}$$

$$R_{ON,SP} = \frac{t_{DR}}{q\mu_n N_D} \quad \Rightarrow \quad R_{ON,SP} = \frac{4V_B^2}{\mu_n \epsilon_S E_C^3}$$


Critical field for breakdown

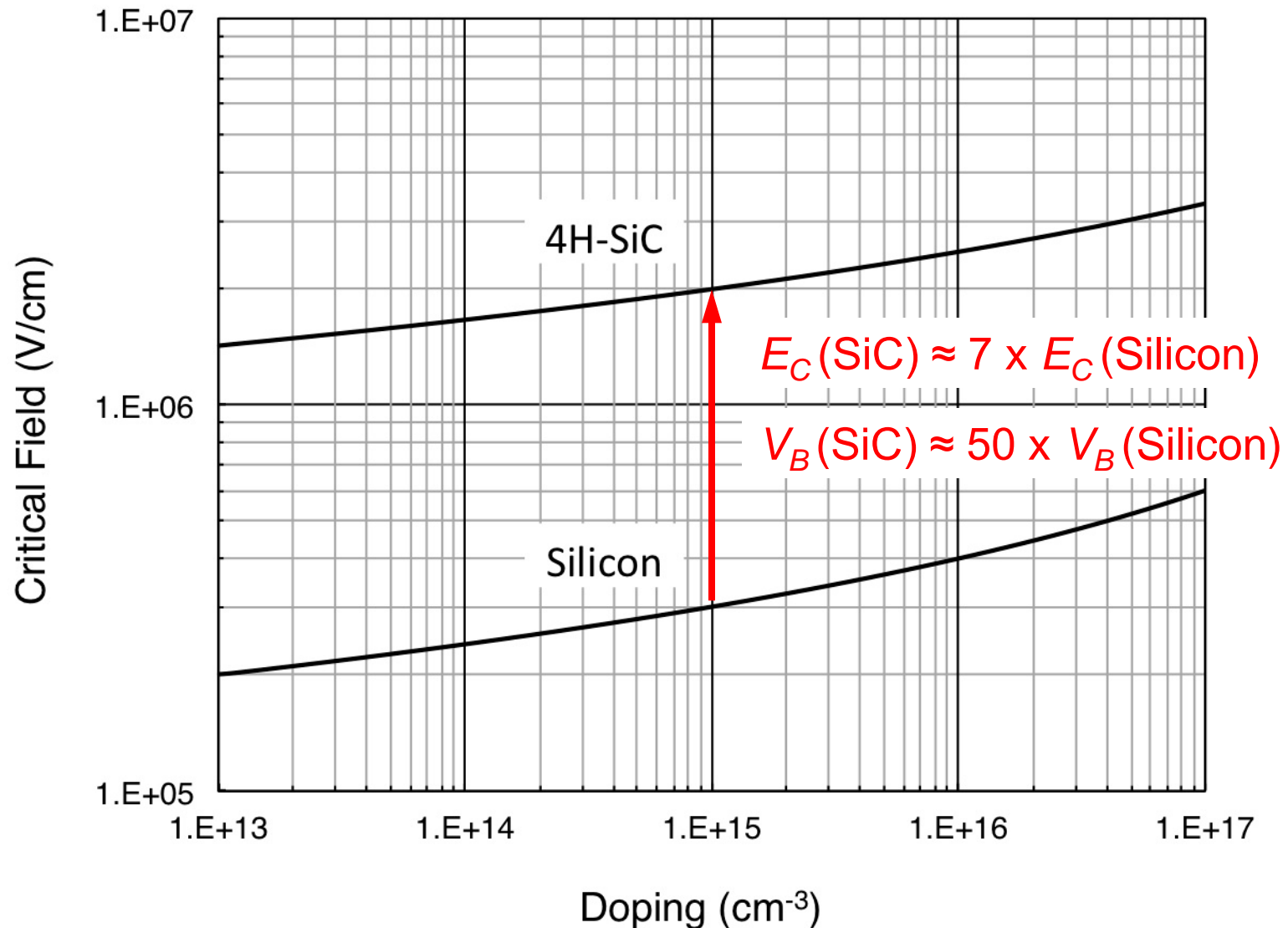

On resistance vs. blocking voltage

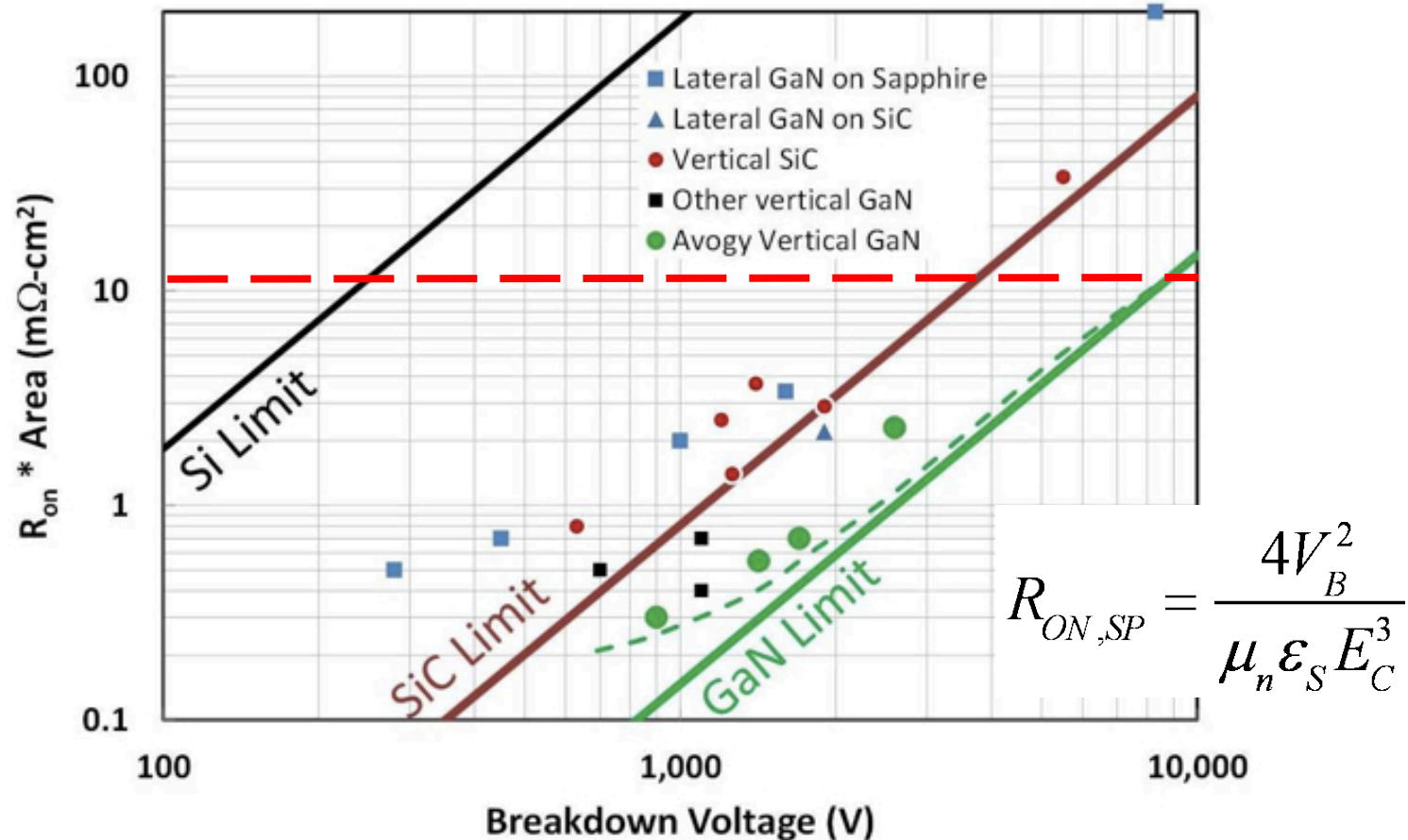


Applications

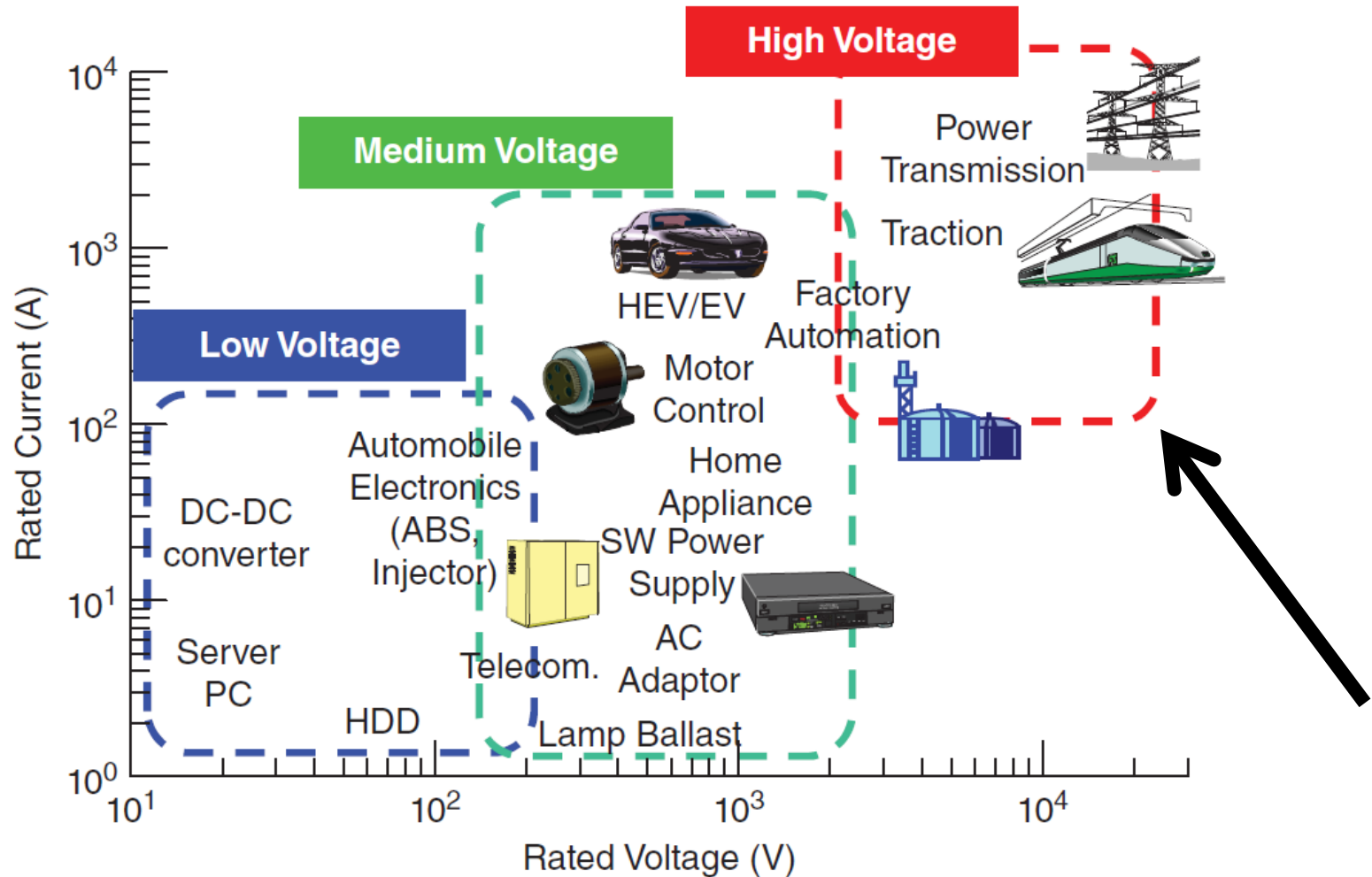


T. Kimoto and J. A. Cooper, *Fundamentals of Silicon Carbide Technology*, Wiley (2014).

DMOSFET

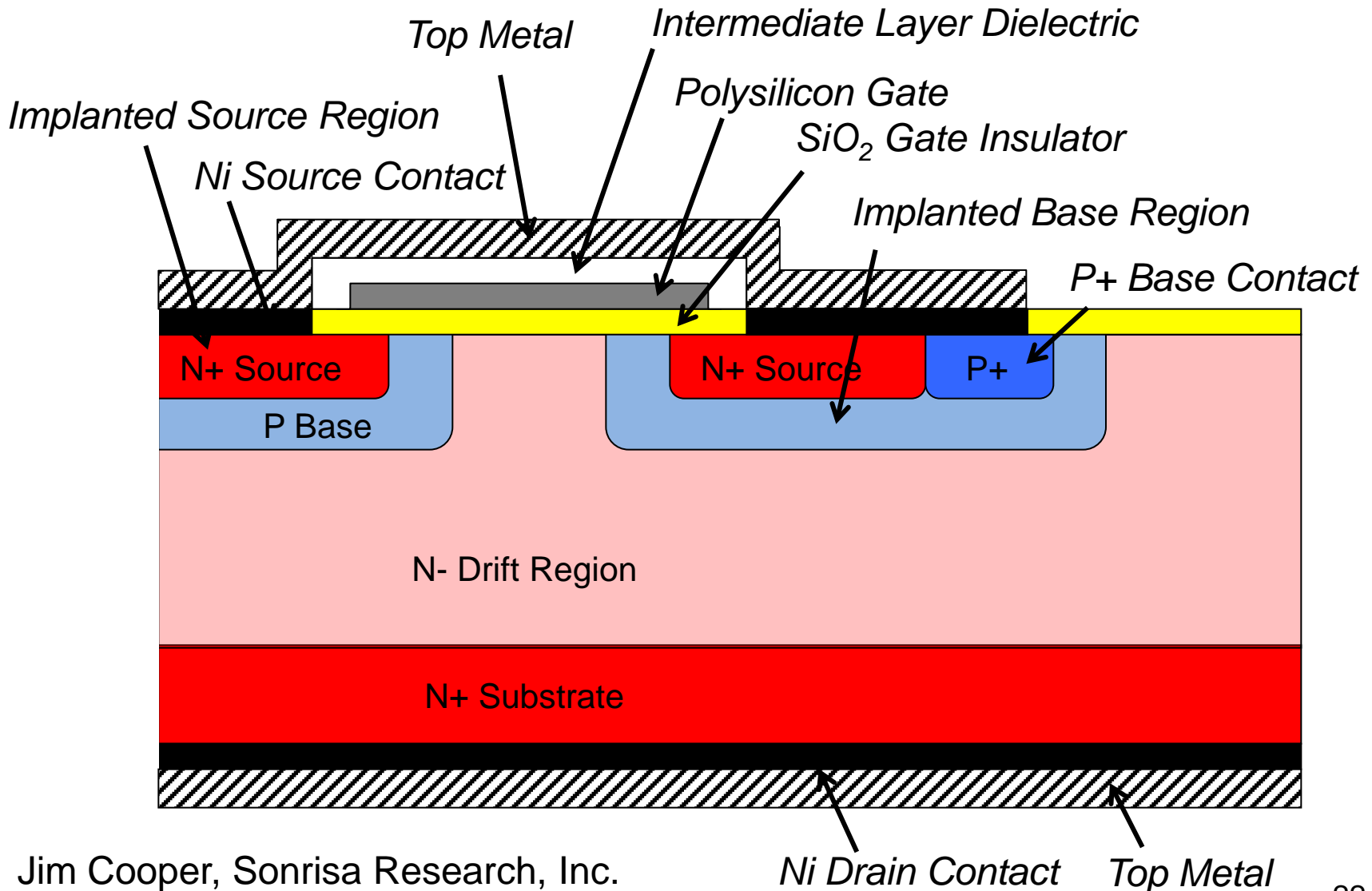

For more information

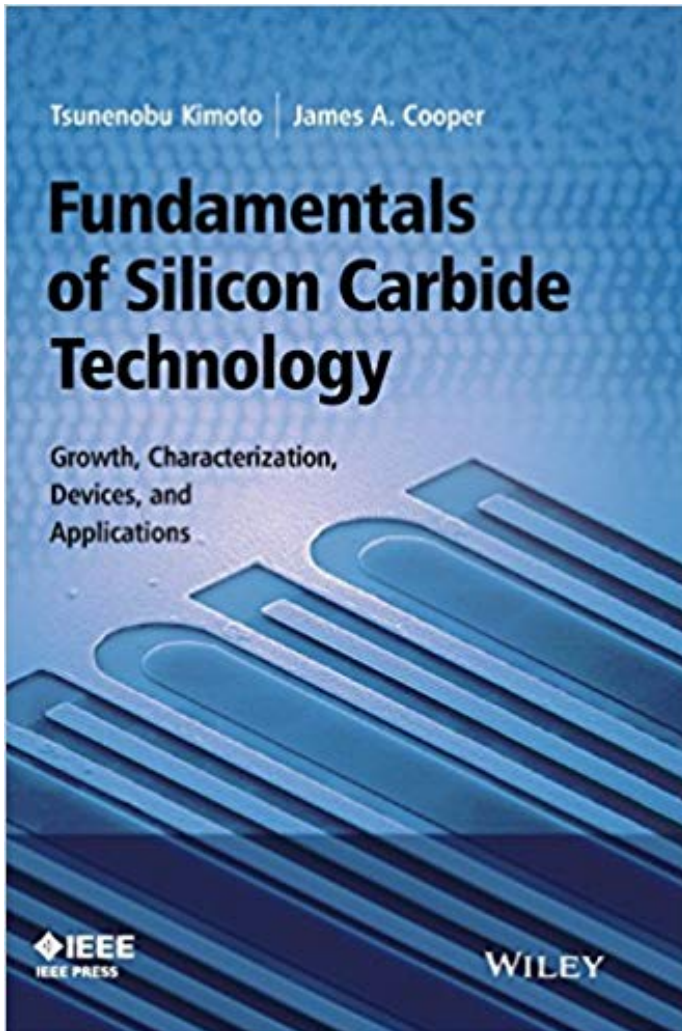

Tsunenobu Kimoto and
James A. Cooper,
*Fundamentals of Silicon
Carbide Technology*,
Wiley (2014).

Summary

- 1) MOSFETs have important applications beyond digital and RF/analog electronics.
- 2) Power MOSFET device geometries and design considerations are much different.
- 3) Power electronics is an important and rapidly advancing field.

Next topic

MOSFETs are not the only type of transistor. In the next lecture, we'll discuss the HEMT – an important RF device.